

DC Circuits

Nathan Warner



Northern Illinois
University

Computer Science
Northern Illinois University
United States

Contents

Basic quantities

- **Planetary model of the atom:** One of the major issues with the planetary model is the idea that electrons whirl around the nucleus in stable, planet-like orbits. That's simply not true. First, the electron inhabits a region of 3D space and does not simply move through a plane

Second, due to the Heisenberg Uncertainty Principle, we can't precisely plot the position and trajectory of a given electron. The best we can do is make a plot of where the electron is likely to be. This is called a probability contour

To understand this concept, imagine that you could record the position of a specific electron relative to the nucleus at a specific time. A moment later you record its new position, a moment after that you record the next position, and so on for thousands of measurements. If you attempted to plot them all, you would wind up with a cloud of dots around the nucleus. This cloud is referred to as an orbital. You wouldn't know how the electron got from one position to the next but you would get a general idea of where it was likely to be. Ultimately, an orbital looks nothing like a planetary orbit.

- **Shells, subshells, and orbitals:** The electron cloud is referred to as an **orbital**.

We note that there are several potential orbitals. Due to quantum physics, only certain orbitals are allowed. The permissible electron energy levels are first grouped into shells, then subshells and finally orbitals. It is important to remember that orbitals indicate the electron energy level. That is, a higher orbital implies a higher energy level. Further, orbitals fill in first from lowest energy level to highest energy level.

- **Charge and current:** Charge is an attractive force denoted by the letter Q and has units of coulombs.

Electrons are negatively charged and protons are positively charged. All electrons and protons exhibit the same magnitude of charge

Further, opposite charges attract while like charges repel, similar to the poles of a magnet.

- **Moving charge:** It is possible to move charge from one point to another. The rate of charge movement over time is called current. It is denoted by the letter I and has units of amps

$$1 \text{ amp} = 1 \text{ coulomb}/1 \text{ second}.$$

Thus, current for current I , charge Q , and time t ,


$$I = \frac{Q}{t}.$$

- **Energy and Voltage:** Energy is defined as the ability to do work. It is denoted by the letter W . The basic unit is the joule

If we were to move a charge from one point to another (for example, separating an electron from an atom), we would have to expend energy to do so

Figure 2.8

Defining voltage as work to move charge.

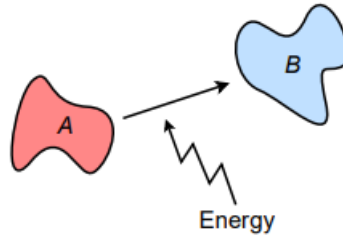

We would say that B has a higher electric potential than A. In other words, there is a potential difference between B and A. We refer to this change as voltage, denoted V , with units volts. One volt is one joule per coulomb.

$$V = \frac{W}{Q}.$$

- V is the voltage in volts,
- W is the energy in joules,
- Q is the charge in coulombs

As you might guess, the bigger the charge to be moved, the greater the energy required

- **Power and efficiency:** Power is the rate of energy usage

$$P = \frac{W}{t}.$$

Measured in watts.

$$1 \text{ watt} = 1 \text{ joule} / 1 \text{ second}.$$

- **The power law:** Recall that

$$I = \frac{Q}{t}, \quad V = \frac{W}{Q}, \quad \text{and} \quad P = \frac{W}{t}.$$

So,

$$P = \frac{VQ}{t} = IV.$$

We call $P = VI$ the **power law**.

- **Efficiency:** Efficiency is the ratio of useful output power to applied power expressed as a percentage

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} \times 100\%.$$

If a device draws 200 watts of power and has a useful output of 120 watts, the efficiency is

$$\eta = \frac{120}{200} \cdot 100\% = 60\%.$$

In this case, the device is wasting 40% of the input power, or 80 watts.

- **amp-hour:** An amp hour (Ah, or ampere-hour) is a unit of measurement used to describe the total electric charge or capacity of a battery.

One amp hour means a battery can deliver a steady current of 1 amp for 1 hour.

The lifespan of a battery is roughly the amp-hour rating over the current draw.

$$\text{Lifespan} \approx \frac{Ah}{I}.$$

Amp-hour is calculated by multiplying current by time

$$Ah = It.$$

It measures the total electric charge a battery can hold or deliver.

- **Resistance and conductance:** Resistance is a measure of how difficult it is to establish a flow of current

Sometimes it is more convenient to use the inverse view of this phenomenon, and instead of referring to how difficult it is to establish a current, we would be interested in how easy it is to establish a current. This is called conductance and it is the reciprocal of resistance. Conductance is denoted by the letter G and has units of siemens (S).

$$R = \frac{1}{G}, \quad G = \frac{1}{R}.$$

- **Resistivity:** The measure of a material's inherent and general ability to restrict current flow is called resistivity. Resistivity is denoted by the Greek letter ρ

All other factors being equal, the higher the resistivity, the greater will be the resistance. Further, the greater the length of the material that the current must pass through, the greater the resistance. Finally, as the surface area of the cross section (i.e. the face) grows, the resistance decreases.

$$R = \frac{\rho \cdot l}{A}.$$

- R is the resistance in ohms,
- ρ is the resistivity,
- l is the length of the material,
- A is area of the face (h times w).

Resistivity is often specified in ohm-centimeters with the length and area similarly specified in centimeters and square centimeters


- **Resistors:** Resistors are **linear bilateral devices**. Being linear, their current-voltage relation can be drawn as a straight line. Bilateral means that the polarity of voltage or direction of current will not matter. In other words, unlike a battery, these devices cannot be inserted into a circuit backwards because either orientation works the same way. If the horizontal axis is voltage and the vertical is current, then the slope of the line yields the conductance

If the x-axis is labeled voltage, and y-axis is labeled current, the steeper the line, the lower its resistance

General purpose resistors use a color code to denote their value and tolerance. Typically, this will involve four color stripes: two for the precision/mantissa, one for the power of ten, and the fourth to indicate the tolerance. For higher precision, a five stripe version may be used with the first three denoting the precision/ mantissa. Alternately, high precision resistors may have their nominal value printed directly on them

 Example of basic four stripe resistor color code.



Color	Numeral
	Black 0
	Brown 1
	Red 2
	Orange 3
	Yellow 4
	Green 5
	Blue 6
	Violet 7
	Gray 8
	White 9
<i>For small resistor values</i> If the multiplier band is gold then divide by 10; if silver, divide by 100.	

Note that the fourth band is spaced away from the others to avoid accidentally reversing the order.

- **Overvoltage (overload voltage):** Overvoltage is a condition where the electrical supply voltage rises above the safe design limit or rated nominal value of a circuit or device
- **Force Sensing Resistor (FSR):** The force sensing resistor consists of two layers of material with a nominal separation distance. It is presented as a flat membrane that is usually round or rectangular, and perhaps with an adhesive backing.


With no force applied, the device shows an extremely high resistance, well into the megohms. As force is applied to the surface, the two layers come into better contact which decreases the net resistance

- **Photoresistor (light dependent resistor (LDR)):** As their name implies, photoresistors are sensitive to changes in light level. They are also called LDRs, short for Light Dependent Resistor

In total darkness the device exhibits a very high resistance. As light levels increase, the resistance decreases.

- **Thermistor:** A thermistor is a device whose resistance is a function of temperature. These devices are available in two basic types. Either PTC, for Positive Temperature Coefficient; or NTC, for Negative Temperature Coefficient. PTC devices show an increase in resistance as temperature increases and NTC devices show a decrease in resistance as temperatures rise. Ideally, these are linear relationships with the plots showing straight lines.
- **Varistor:** Varistors are used as limiting devices, primarily to suppress unwanted voltage spikes in electronic equipment. The varistor is a unique device in that it has a highly nonlinear current-voltage characteristic.

Remember, when plotted with the voltage on the horizontal axis, the slope of the line represents the conductance. Consequently, the varistor shows a region of near zero conductance or extremely high resistance (the horizontal section), and two sections that are nearly vertical, which indicate extremely high conductance or near zero resistance. This characteristic allows the varistor to act as a limiting device.

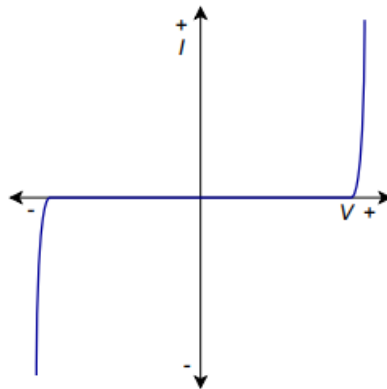


- **Schematic symbols:** Clearly, it would not be practical to create circuit drawings (schematics) using pictures of the actual devices. Instead, we use simple schematic symbols to represent them. There are two widely used schemes: ANSI (American National Standards Institute) and IEC (International Electrotechnical Commission). For many electronic components the ANSI and IEC versions are the same, but there are notable differences. ANSI tends to dominate in North America (surprise!) while IEC tends to dominate elsewhere.

Figure 2.38 shows the symbols for DC current and voltage sources. The long bar at the top of the voltage source is the positive terminal while the shorter bar at the bottom denotes the negative terminal. For the current source, the arrow points in the direction of conventional current flow. If the source is adjustable, it will often be shown with a diagonal arrow drawn through it. In some schematics, a DC voltage source will simply be drawn as a “connection dot” or node with the voltage labeled. It is assumed that the other end of the source is tied back to the system common or ground.

Figure 2.38

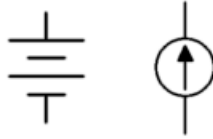
Voltage (left) and current source schematic symbols.



Speaking of ground, there are three different symbols used for a circuit's common connection point. These are: earth ground, chassis ground and signal or digital ground. These are shown in Figure 2.39. Earth ground is used when the circuit common is tied back to true earth (e.g., to the third pin on an AC receptacle). Chassis ground is a more generic term which would represent a common reference point that did not go back to true earth (e.g., a portable device). Finally, digital or signal ground is used to distinguish between common points where they might be separated for noise or interference concerns (e.g., a sensitive analog signal common separate from a digital logic common).

Figure 2.39

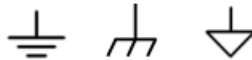*Schematic symbols for ground.
(L-R) earth, chassis, signal.*



The symbols for resistors and other resistive devices vary considerably between ANSI and IEC versions. ANSI uses a zig-zag line while IEC uses a simple rectangle

One final note about component values: As decimal points are easy to lose on photocopies or small display screens, engineering notation multipliers are sometimes placed in the position of a decimal point. For example, a 4.7 k Ω resistor may be listed as simply 4k7.

Series Resistive Circuits

:


- **Intro:** Benjamin Franklin (pictured in Figure 3.1) began experimenting with the phenomenon of electricity in 1746. In 1752 he performed his famous kite experiment proving that lightning is a form of electricity by capturing charge from storm clouds in a leyden jar (an early form of an electrical charge storage device).

At this time the modern concept of an atomic model with electrons and protons did not exist and electricity was conceived of as a sort of fluid. Franklin surmised that the “electrical flow” moved from positive to negative. This idea was accepted and became the conventional view. Today we call this idea **conventional current flow**. In this model, current flows from a more positive voltage to a less positive voltage. We know now that the electron is the charge carrier in metals and the electrons travel in the reverse direction. Essentially, Franklin guessed wrong. Electrons move from a lower potential to a higher potential. We call this model **electron flow**. For most work, engineers and technicians use conventional flow, although in some cases, such as the explanation of semiconductors, electron flow is easier to visualize for some people. In short, conventional flow exists for historical reasons, and it is the model used for most analyses, including this text.

You might think the current direction would make a big difference in an analysis; after all, it certainly makes a big difference if you drive a car in the wrong direction. It turns out that both forms will achieve the desired results, we just have to be consistent with the usage.

To better understand this, consider that the movement of a net negative charge in one direction can be thought of as a movement of a net positive charge in the other direction. That is, the movement of an electron creates a “hole” where it used to be and that hole is net positive.

Figure 3.2
Electron versus hole flow.

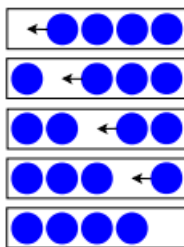

Here we start at the top with a tube of identical marbles, all pushed to the right. In each step below it we move a marble to the left, mimicking the flow of electrons in a circuit. When we reach the bottom, each marble has been pushed left by one place. We can also arrive at the bottom drawing by simply taking the right-most marble in the top drawing and inserting it to the extreme left by jumping over the other three marbles. Here’s the important bit: instead of imagining the marbles moving left, we

can also think in terms of “negative space” and imagine the empty slot moving to the right. That’s hole flow. The two views are functionally identical as they lead to the same outcome.

- **Circuits:** The word circuit comes from the Latin root *circ*, meaning “ring” or “around”. An electrical circuit consists of at least one ring or loop through which current flows. For example, if we have a battery attached to a lamp the current exits the battery, flows through the lamp, and then returns to the other side of the battery creating a loop or completed circuit. Without a path back to the battery, current will not flow. Thus, if we cut one of the wires connecting the battery and lamp, there is no path for current and no current flows. This is referred to as an open circuit and is a common fault that occurs when electronic systems are dropped or struck forcefully. Obviously, this will tend to render the circuit unusable. In this example, the lamp will not illuminate.

The opposite of the open circuit is the short circuit. In a short circuit, an unintended alternate path for current flow exists and this also can create a malfunction. In the case of our battery and lamp, a short circuit can occur if a piece of wire or metal accidentally fell across the terminals of the lamp. The current would then have a high conductance (i.e., low resistance) path around the lamp. The vast majority of the current would take this low resistance path instead of the higher resistance path presented by the lamp. The result would be that the lamp would not light. In either the open or short case, the light does not function but there is an important difference: for the short circuit, excessive current will flow out of the battery because there is little to resist the flow of current. Thus, the battery will be drained very quickly. For the open, no current flows and thus the battery is not drained.


- **Series connections:** In general, a series connection is any connection of components configured such that the current through each component must be the same

Inside each of the lettered boxes would be a component such as a resistor or a voltage source. Note that for each component, there is one entrance point and one exit point. No matter which box you pick, the current flowing through it must be the same as the current flowing into the next box or out of the preceding box, and it doesn’t matter if you follow this path in a clockwise or counterclockwise fashion. Thus, this entire configuration is a series connection. The idea that current is consistent throughout should be selfevident. After all, the only way the current through, say, item B could be different from that flowing through item C or D is if some of it somehow “disappeared” along the way by magic. It is important to remember that consistent current is the hallmark feature defining a series connection:

It is possible that only a portion of a circuit exhibits a series connection.

Consider the more complex diagram presented in Figure 3.5. Some of these items are in series and some are not. For example, items A and B are in series with each other but not in series with the remaining items. Why? Because if we imagine the current flowing through A and then through B they must be the same, however, once beyond B, the current could split and flow down other branches: a portion entering C, a portion entering D and the remainder flowing into E. On the other hand, items C and F are in series with each other because whatever current is flowing through one of them must be flowing through the other. Thus, items A and B are in series with each other and items C and F are in series with each other, although all four are not in series as a group.

Figure 3.5
A more complex configuration.

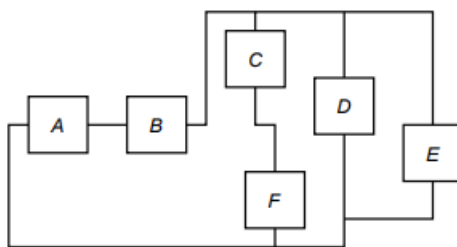

It is possible that no two items in a circuit are strictly in series. Further, just because the currents through two items happen to be the same, that does not necessarily mean they are in series. Identical currents could be just a by-product of the component values chosen

Even if items D and E in Figure 3.5 have the same numeric value for current, we would not say that they are in series, anymore than we would say that any two people with the same last name would have to be siblings.


- **Combining Series Components:** Typically, a series connection will include multiple resistors.

Recall that resistors add

$$R = \frac{\rho \ell}{A}$$

resistance. If we consider two identical resistors placed in series, one after the other the effective length would double while keeping the resistivity and area unchanged. The combined result would be a doubling of the resistance of just one of them.

Figure 3.6
Resistors in series.

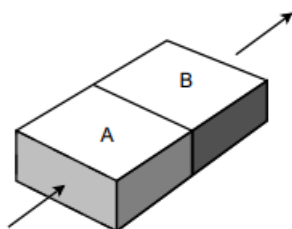

If we then generalize this to two arbitrary resistors of identical resistivity and area, the lengths would dictate the resistance of each, and the combined lengths would then


reflect the resistance of the pair.

$$R = \frac{\rho(\ell_1 + \cdots + \ell_n)}{A} = \frac{\rho}{A}(\ell_1 + \cdots + \ell_n)$$

Thus we find that the equivalent resistance of a group of series resistors is their sum:


$$R_{\text{total}} = R_1 + R_2 + \cdots + R_n.$$

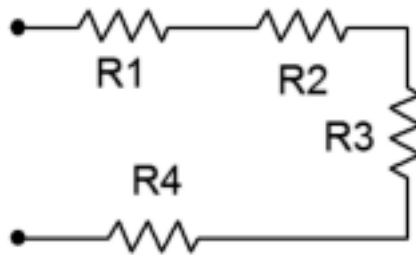Consequently, as resistors in series add, total resistance may be found by summing the individual resistors.



Multiple voltage sources in series may also be added, however, polarities must be considered as opposing voltages partially cancel each other (i.e., adding a negative).

Figure 3.8
Voltage sources in series.

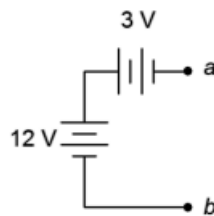

If we use point b as our reference, by inspection the top of the 12 volt source is 12 volts above point b (reminder, the long bar denotes the positive terminal). Also, by inspection, the right side of the 3 volt source (point a) is negative with respect to its left side. As the left side of this source is connected to the positive terminal of the 12 volt source, then it too must be 12 volts above point b. As its right side is 3 volts less than this side, point a must be 3 volts less than 12 volts, or 9 volts above point b. Thus

$$V_{ab} = 9\text{volts..}$$

Chasing this further, if the 3 volt source had been flipped so that it had the same polarity as the 12 volt source (positive toward the right) then $V_{ab} = 15$ volts. If the 12 volt source had been flipped (positive toward bottom) with the 3 volt source as drawn originally, then $V_{ab} = -15$ volts. If both sources had been flipped then $V_{ab} = -9$ volts. Finally, if point a had been taken as the reference then these four potentials would have the opposite polarity because, by definition, $V_{ba} = -V_{ab}$.

In contrast to voltage sources, differing current sources are not placed in series as they would each attempt to establish a different series current, a practical impossibility

- **Generality:**

$$\text{Effect} = \frac{\text{cause}}{\text{opposition}}.$$

- **Ohm's law:** We have

$$V = IR.$$

Or,

$$R = \frac{V}{I}.$$

Note that from this, we get

$$P = I^2 R = \frac{V^2}{R}.$$

- **Kirchoff's Voltage Law (KVL):** Along with Ohm's law, the key law governing series circuits is Kirchhoff's voltage law, or KVL. Named after nineteenth century German physicist Gustav Kirchhoff, this law states that the sum of voltage rises and voltage drops around a series loop must equal zero (the rises and drops having opposite polarities). Alternately, it may be reworded as the sum of voltage rises around a series loop must equal the sum of voltage drops

$$\sum V \uparrow = \sum V \downarrow.$$

- **Voltage divider rule (VDR):** An outgrowth of KVL is the voltage divider rule (VDR). In a series connection, the current is the same through each component. Thus, the voltage drops in a series connection must be directly proportional to the size of the resistances: the larger the resistor, the larger its voltage, and the larger its share of the total voltage applied to the series connection. Thus, the voltage across any resistor must equal the net supplied voltage times the ratio of the resistor of interest to the total resistance:

$$V_{R_x} = E \cdot \frac{R_x}{R_{\text{total}}}.$$

This is just two Ohm's law calculations:

$$V_{\text{total}} = E = IR_{\text{total}} \implies I = \frac{E}{R_{\text{total}}}.$$

Then, for a particular resistor R_x :

$$V_{R_x} = IR_x = \frac{E}{R_{\text{total}}} \cdot R_x = E \cdot \frac{R_x}{R_{\text{total}}}.$$

It is worth pointing out that "the resistor of interest" can, in fact, be the sum of multiple resistors in series.

While VDR is not required for any particular analysis, it serves two purposes: first, it saves some time because it skips over the computation of current, and second, it reinforces the ideal of a proportional division of voltage in a series connection. For example, if there are two resistors in series and one of them is twice the size of the other, then it must be the case that the larger resistor sees twice the voltage of the smaller resistor.

- **Series analysis:** Ohm's law, Kirchhoff's voltage law, the voltage divider rule and series component combinations are the tools we will use to solve general series circuit problems. There are multiple techniques for analyzing these circuits:
 - If all voltage source and resistor values are given, the circulating current can be found by dividing the equivalent voltage by the sum of the resistances. Once the current is found, Ohm's law can be used to find the voltage drops across individual resistors. Alternately, the individual voltage drops can be found using the voltage divider rule. At that point, power law can be used to find the power dissipation in each resistor or the power developed by the source(s).
 - If the circuit uses a current source instead of a voltage source, then the circulating current is known and the voltage drop across any resistor may be determined directly using Ohm's law.
 - If the problem concerns determining resistance values, the basic idea will be to use these rules in reverse. For example, if a resistor value is needed to set a specific current, the total required resistance can be determined from this current and the given voltage supply. The values of the other series resistors can then be subtracted from the total, yielding the required resistor value. Similarly, if the voltages across two resistors are known, as long as one of the resistance values is known, the other resistance can be determined using either the voltage divider rule or Ohm's law.
- **Node voltage:** A node voltage is the voltage at a given point with respect to some other point, normally ground

Note that as we treat connecting wires ideally (having no resistance), a node is the entire connection wire, not a specific location on it. Normally, simulators will automatically number each node in a circuit with ground being node 0. This method skips the entire business of inserting virtual meters in the circuit and reduces schematic clutter.

- **Voltage rise and voltage drop:** A voltage rise occurs when you move from a lower electric potential to a higher electric potential:

A voltage drop occurs when you move from a higher electric potential to a lower electric potential:

- **The Importance of Polarity:** A key item of importance when analyzing series circuits, or indeed any electrical circuit, is noting the polarity of the voltages.

Determining polarity for voltage sources is easy as their polarity is fixed (positive is always at the "long bar" and negative at the "short bar"). The polarity of any resistor will depend on the direction of current flow. To avoid confusion we will use the following standard:


- Where conventional current enters a resistor, we label this point with a plus sign, and where the current leaves, a minus sign.

- During analysis, moving from plus to minus is a voltage drop. That is, we are moving from a more positive or higher potential to a less positive or lower potential, thus “dropping” voltage.
- Similarly, traversing from minus to plus is a voltage rise.

Remember, Kirchhoff’s voltage law states that the sum of voltage rises around a series loop must equal the sum of voltage drops.

Along with determining the voltage across single resistors, we are often interested in determining the voltage between arbitrary points in a circuit. These may span several components. It is imperative that we know the polarities of the individual voltages in order to determine the voltage between any two circuit points.

Figure 3.21
A multi-source, multi-resistor series circuit.

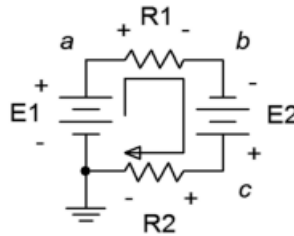

Here, the two voltage sources, E_1 and E_2 , aid each other because they are both trying to establish a clockwise current. This produces a net voltage of $E_1 + E_2$. Their polarities are fixed. The current direction will be as drawn because conventional current flows out of the positive terminal of a voltage source. The value of this current will be

$$I = \frac{E_1 + E_2}{R_1 + R_2}$$

via Ohm’s law.

Knowing the direction of current, the polarities of the voltage drops across the two resistors may be found. The point where the current enters the resistor is positive, and negative where it exits. Once these are labeled, either Ohm’s law or the voltage divider rule can be used to determine the voltages developed across the two resistors. Note that KVL states that the sum of these two resistor voltages must equal the net supplied voltage, or $E_1 + E_2$ in this case.


To determine the voltage from point a to point c , or V_{ac} , we start at point a and sum the voltage drops and rises until we get to point c . Here, the voltage across R_1 shows up as a drop

The result is the voltage across R_1 minus the voltage across E_2 .

Depending on the specific values, the sum may wind up being either a positive or negative value. If it's positive, this signifies that point a is at a higher potential than is point c . Conversely, if it's negative, this signifies that point a is at a lower potential than is point c .

To illustrate the importance of voltage source polarity, consider the series circuit shown in Figure 3.22.

Figure 3.22
Series circuit with altered polarity.

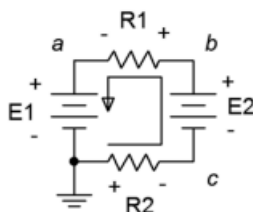

The two voltage sources oppose each other because their positive terminals are connected through R_1 , rather than one source's positive terminal aiding the other source.

Assume $E_2 > E_1$.

Following the indicated current direction around the loop:

- Passing through E_2 from c to b produces a voltage rise of $+E_2$.
- Passing through E_1 from a downward produces a voltage drop of $-E_1$.

Therefore, the net voltage driving the circuit is

$$E_{\text{net}} = E_2 - E_1.$$

The current is therefore

$$I = \frac{E_2 - E_1}{R_1 + R_2}.$$

Both resistors are in series, so the same current flows through them.

Because E_2 is the stronger source, conventional current leaves its positive terminal at b . It then travels:

$$b \rightarrow R_1 \rightarrow a \rightarrow E_1 \rightarrow R_2 \rightarrow c \rightarrow E_2.$$

Thus, current passes:

- Through R_1 from right to left.
- Through E_1 from its positive terminal to its negative terminal.
- Through R_2 from left to right.

A source delivers energy when conventional current leaves its positive terminal. Current leaves the positive terminal of E_2 , so E_2 supplies power.

Current enters the positive terminal of E_1 , so E_1 absorbs power.

$$P_{E_1} = E_1 I.$$

If E_1 represents a rechargeable battery, that absorbed power corresponds to charging. If it is an ideal voltage source, “charging” simply means that it is absorbing energy.

- $E_1 < E_2$: current flows as drawn.
 - $E_1 > E_2$: current flows in the opposite direction.
 - $E_1 = E_2$: the ideal circuit has zero current.
- **Potentiometers and Rheostats:** Some applications require the use of variable resistances. One example is a basic volume control, but other examples include equipment calibration and user adjustable parameters such as the bass, treble and balance controls on a home audio system. Adjustable resistances fall under two categories, potentiometers and rheostats. Generally, these would be the same physical device, with the application and usage determining its name.

A potentiometer is a resistor with three leads. Along with the typical end leads, there is a third lead referred to as the wiper or tap. This third lead is connected to a small metallic arm that makes contact with the resistive material and which can be moved along the length of the material. Potentiometers, or pots for short, often are formed in a circular shape (rotary travel) but they can also be in the form of a straight line (linear travel)

The larger circular units with shafts and the straight unit at the top are designed to be adjusted by the end user (appropriately stylish knobs being attached to said shafts, of course), while the smaller units are intended to be adjusted only by a technician (note the small adjustment screw slots intended to receive fine screwdrivers). The smaller units are designed to be mounted directly on a printed circuit board while the user adjustable units are mounted on a front panel, and have wiring lugs instead of straight leads.

A pot can be visualized as two resistors in sequence with a tap between them. The total resistance never changes. What does change is the ratio of the two pieces.

$$R_{AB} = R_{AW} + R_{WB}.$$

Figure 3.30
Schematic symbol for a potentiometer, with labels.



- **Ganged potentiometers:** As a result, potentiometers are very useful as controllable voltage dividers (hence the name). Sometimes it is desirable to control two signals simultaneously from a single knob (e.g., one volume knob for a hi-fi stereo controls both the left and right channels). For this application, multiple resistive elements can be stacked and use a common shaft to control all of the wiper arms in tandem. These are known as **ganged potentiometers**.


Finally, unlike fixed resistors, pots are available in limited sizes. Typical values use multiples of 1 or 5 for the total resistance

The output voltage at the wiper of a potentiometer changes because the wiper splits the total resistive track into two smaller resistor sections, and the voltage drops across each section in direct proportion to its length

- **Rheostat:** If only the wiper and only one of the two end terminals is used, then the device is referred to as a rheostat. Rheostats are often used to limit current. The value of the rheostat ranges from 0 up to the nominal value of the potentiometer.

Figure 3.31

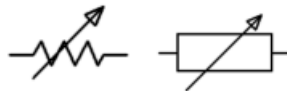Schematic symbols for a rheostat: ANSI (right) and IEC (left).




Parallel resistive circuits

- **The parallel connection:** In a parallel connection the voltage is the same across each component.

Figure 4.1

A parallel configuration.

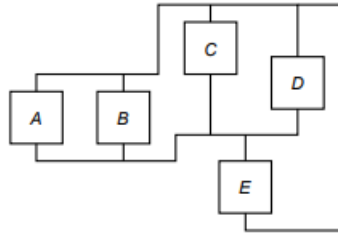


Although it may be drawn oddly, there are only two common connection nodes in this configuration: one along the top and the other along the bottom

If we were to take a voltmeter and place it across any of these blocks, the meter would read the same voltage across each because the probes are always contacting the same two nodes

Figure 4.2

A more complex configuration.

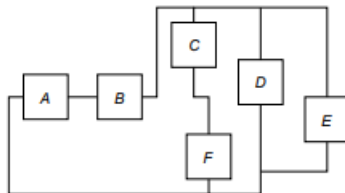


In this layout some elements are in series and some are in parallel. Only elements D and E are strictly in parallel here as they are the only two that connect to the same two nodes, and thus must see the same voltage.

Items C and F might at first appear to be in parallel with them but upon closer inspection it should be noted that C and F are in series with each other. That is, C and F will split the voltage that D or E sees, in accordance with the voltage divider rule. In other words, it is not true that the voltage across C or across F must be the same as the voltage across D or E

- **Combining Parallel Components:** Our first step is to determine how to combine parallel components in order to create a single equivalent component. Unlike series connections, this can be a little more time consuming.
- **Sources in parallel:** First, voltage sources are not placed in parallel as a general rule

Figure 4.3

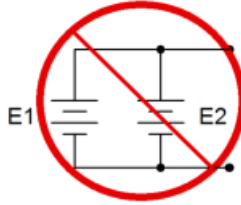Do not place voltage sources in parallel.




The reason is because a parallel connection requires the same voltage across each component. This would be impossible to achieve with each source trying to maintain a different voltage across the same two nodes. This may result in damage to the sources (e.g., exploding batteries). The main exception to this rule is if the sources have the same potential and the goal is to extend operational life (e.g., multiple D cell batteries in parallel).

- **Current sources in parallel:** When it comes to current sources, they may simply be added together, however, like series voltage sources, polarity is important. Referring to the three parallel current sources in Figure 4.4, the middle and right sources are pumping current into the top node while the left source is feeding the bottom node. You can also think of the left source as draining the top node. Thus, these three sources together behave like a single source of five amps feeding the top node (eight amps in, three amps out).


Figure 4.4

Current sources in parallel.

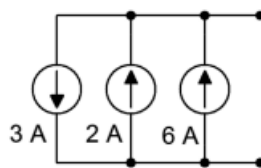

- **Resistors in Parallel:** When placed in parallel, resistor values do not add the way they do in series connections.

Figure 4.5
Resistors in parallel.

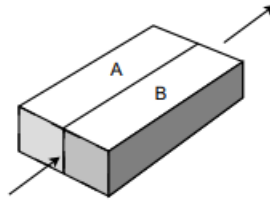

Recall that

$$R = \frac{\rho l}{A}.$$

Notice that two of the same resistor in parallel would double the area, which resistivity and length unchanged. Thus, the resistance is halved. So, we see that placing resistors in parallel results in a decrease in net resistance, the opposite of the series case.

Recall that **conductance** G is given by the reciprocal of resistance

$$G = \frac{A}{\rho l}.$$

Now we can see that the increase in area creates a proportional increase in conductivity. If we generalize this for N resistors we find that the equivalent conductance of a group of parallel resistors is their sum

$$G_{\text{total}} = G_1 + \cdots + G_N.$$

Thus,

$$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \cdots + \frac{1}{R_N}.$$

Hence,

$$R_{\text{parallel}} = \frac{1}{\frac{1}{R_1} + \cdots + \frac{1}{R_N}}.$$

For N resistors of equal resistance,

$$R_{\text{parallel}} = \frac{1}{\frac{N}{R}} = \frac{R}{N}.$$

Also, consider two parallel resistors R_1 and R_2 , with $R_1 < R_2$. Then,

$$R_P = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}.$$

Consider R_1 alone,

$$R_P = \frac{1}{\frac{1}{R_1}} = R_1.$$

Now, consider what happens when we add R_2 . Since resistance is non-negative, adding $1/R_2$ admits

$$\frac{1}{R_1} + \frac{1}{R_2} > \frac{1}{R_1}.$$

Thus,

$$\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} < \frac{1}{\frac{1}{R_1}} = R_1.$$

Thus, the combined resistance is smaller than the smallest resistor in the parallel series.

- **Product-Sum Rule:** For two resistors,

$$R_P = \frac{R_1 R_2}{R_1 + R_2}.$$

It is only applicable to two resistors, however, it can be used repeatedly on pairs of resistors within larger groups instead of using

Now, suppose we write

$$N = \frac{R_2}{R_1},$$

so that

$$R_2 = \frac{N}{R_1}.$$

Now,

$$R_P = \frac{R_1 N R_1}{R_1 + N R_1} = \frac{N}{N + 1} R_1.$$

This is useful for quick estimates of parallel resistor pairs. If we have a resistor ratio of 3:1, then the equivalent would be 3/4ths the value of the smaller resistor. For a $24k\Omega$ and a $8k\Omega$, the equivalent would be a $6k\Omega$ resistor.


- **Kirchhoff's Current Law (KCL):** Just as Kirchhoff's voltage law is a key element in understanding series circuits, Kirchhoff's current law (KCL) is the operative rule for parallel circuits. It states that the sum of all currents entering and exiting a node must sum to zero. Alternately, it can be stated as the sum of currents entering a node must equal the sum of currents exiting that node. As a pseudo formula:

$$\sum I \leftarrow = \sum I \rightarrow .$$

Recall that a node is a connection area wherein the voltage is the same

Figure 4.7

A simple parallel circuit.

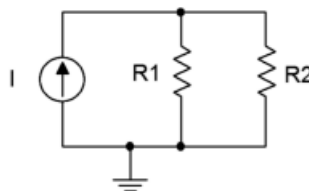

We see that there are two nodes in a parallel configuration. For each of these nodes, whatever currents flow in must be balanced by the same total current flowing out.

There is a current source feeding the top node. At the three-way connection with R_1 and R_2 , KCL along with Ohm's law dictate that the incoming current from the source must split with one portion exiting by flowing down through R_1 and the remainder exiting by flowing down through R_2 .

At the bottom node (ground) these two resistor currents must combine and equal the current that is being drawn back into the current source, which must be the same as the current originally produced by the source. This is perfectly sensible because it would be impossible for the current source to establish two different currents; one at its input and the other at its output. To assert otherwise would be a little like saying you're two different heights depending on whether you measure from your toes up to your head versus from your head down to your toes. Thus, a simplistic way of stating KCL is "What goes in must come out"

- **The Current Divider Rule (CDR):** Just as series circuits follow the voltage divider rule (voltage dividing in proportion to resistance), parallel circuits follow the current divider rule which states that current divides in reverse proportion to resistance (i.e., in direct proportion to conductance).

First, we note that the voltage across the pair must equal the entering current times the effective resistance of the pair.

$$V = I_T \frac{R_1 R_2}{R_1 + R_2}.$$

The current through each of the resistors must be this voltage divided by the corresponding resistance. For the current through R_1

$$I_{R_1} = \frac{V}{R_1} = I_T \frac{R_2}{R_1 + R_2}.$$

Similarly, for the current through R_2 :

$$I_{R_2} = I_T \frac{R_1}{R_1 + R_2}.$$


Hence,

$$I_X = I_T \frac{R_Y}{R_X + R_Y}.$$

This rule is convenient in that you don't have to compute the parallel equivalent resistance, but remember, it is valid only when there are just two resistors involved.

- **Fuses and circuit breakers:** Most electrical and electronic devices are designed to run off of a constant voltage source. As such, parallel connections are ideal when a variable number of devices are to be powered because, unlike a series connection, each device will see the same voltage rather than having that voltage split among them.

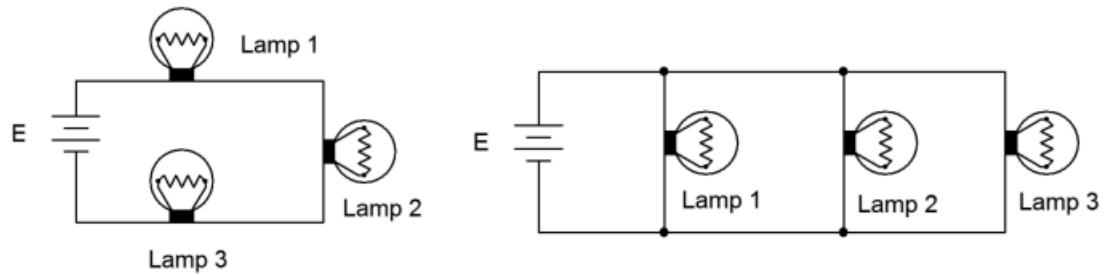There is another advantage to parallel connection. Consider



Typically, when a lamp fails, it fails creating an open. If any of the lamps in the series connection fails, current in the loop is interrupted and all of the lamps go out. In contrast, if one of the lamps in the parallel connection fails, the remaining lights will stay on. Further, in the series connection, there is no immediate way to determine which lamp has failed as none of them will be lit. Each lamp has to be tested in turn to determine the faulty unit. In the parallel system, it is obvious which lamp has failed because that's the one that's out.

In a home, school or commercial setting, any number of devices may be plugged into wall sockets with the expectation that each unit will receive the same voltage and operate correctly due to the parallel nature of the system. As convenient as this is, there is a practical problem. Every device that is added to the system presents another path for current flow. Due to KCL, this means that the total current drawn from the source must increase. This creates a potential problem because if too much current is drawn, there can be an appreciable voltage drop across the wires feeding the outlets as they can no longer be assumed to be zero ohms. This lowered voltage may present a problem for the attached devices, but more importantly, the large current results in unexpected heating of the wires because of the power dissipation in them (I^2R) and creates a possible fire hazard. Consequently, we must include some method to limit the current to a safe maximum value.

Adding another load in a parallel circuit increases the total current drawn from the source because it creates a new, separate path for electricity to flow. Each load you add creates an independent branch connected across the same voltage source.

The power source provides the same push (voltage) to every branch. Each new load draws its own separate share of current based on its own resistance

According to Kirchhoff's Current Law, the total current leaving the source is the sum of the currents going through each individual branch. When you add another branch current to the total, the overall sum goes up

Because there are more pathways for the charge to move through, the overall or equivalent resistance of the entire circuit actually decreases.

Since the resistance decreases,

$$I = \frac{V}{R}$$


increases. The common approach is a fuse or circuit breaker. These devices are placed between the voltage source and the various loads, and see their combined current. If this current becomes too great, the device interrupts the current flow by opening the circuit. Nothing will operate but nothing catches fire, either.

Fuses are used typically in electronic systems, motors, automotive subsystems and the like. Whether they're the cylindrical type found in electronic instrumentation or the blade type common in automobiles, fuses are one-shot devices. They consist of a fine wire or metal link that will heat up and melt if it experiences too high of a current. Upon melting, circuit continuity is lost and current flow stops. This is called a "blown" fuse. The fuse will then need to be replaced once the problem has been fixed (i.e., whatever it was that caused excessive current to flow in the first place).

Fuses have a nominal current rating, for example, two amps. This does not mean that as soon as two amps is reached, the fuse blows. It will take some time for the fuse to heat up. The higher the current is above the nominal rating, the faster the fuse will blow.



Figure 4.21
*Schematic symbols for fuses:
IEC (top and middle), ANSI
(bottom).*

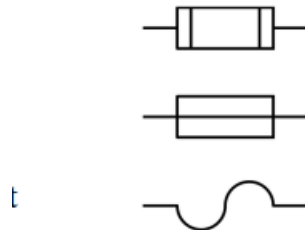

Fuses are also available in fast-blow and slow-blow forms. Fast-blow fuses will activate many times faster than standard fuses while slow-blow types will require much longer to activate (this prevents the fuse from activating accidentally with certain kinds of loads that exhibit a high initial startup current but that falls back to a more modest level once running smoothly, such as a motor).

Fuses are generally inexpensive and effective. The obvious downside to a fuse is that they need to be replaced once they do their job. A circuit breaker solves this problem.

A circuit breaker, or just breaker for short, can be thought of as a resettable fuse. Breakers do not have a melting link that interrupts current flow. Instead, a breaker operates like an intelligent switch: if the current is too large, the switch is thrown open. The operator can then fix the problem and reset the breaker (i.e., return the switch to the operating position).


Figure 4.22
*Residential circuit breakers
including cutaway view.*



Series-Parallel Resistive Circuits

- **Intro:** The key to analyzing basic series-parallel circuits is in recognizing portions of the circuit, or sub-circuits, that exhibit a series or parallel configuration by themselves, and then applying the series and parallel analysis rules to those sections. Ohm's law, KVL and KCL may be used in turn to “chip away” at the problem until all currents and voltages are found. As individual voltages and currents are determined, this makes it easier to apply these rules to determine other values. Given this observation, the number of potential solution paths tends to grow exponentially as the number of components increases. As a consequence, when faced with the same circuit, six people may solve it six different ways, no particular way being more or less correct than any other. The only thing we can say is that some solution paths might be more computationally efficient than others, meaning they take less work
- **Series-Parallel Connections:**

Figure 5.1
A series-parallel
configuration.

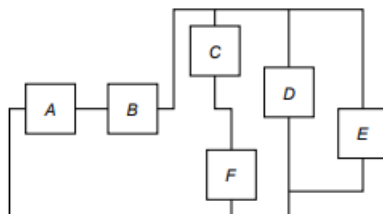


It should be obvious that this system is neither a simple series connection nor a simple parallel connection, but rather some combination of the two. In order for it to be series, the current through each component would have to be the same. This does not have to be true here. Consider the connection node directly above block C. This also connects to items B, D and E. All we really know about that node is that there are four paths leading to it and that the four associated currents must sum to zero, thanks to KCL. There is nothing that requires the current through, say, block D to be the same as that through block E. Similarly, there is nothing that stipulates that the voltage across block C must be the same as that across block F. After all, that is the hallmark of a parallel configuration, and that would require those two blocks to be connected to the same two nodes, which they aren't.

Notice some of the components are in series among themselves, and some are in parallel among themselves. We might recognize these groupings as sub-circuits.

For example, it is true that blocks A and B are in series with each other because the current through one of them must be the same as the current through the other. The same is true of blocks C and F; they are in series with each other. Similarly, we can say that blocks D and E are in parallel with each other because they must see the same voltage as they are each connected to the same two nodes

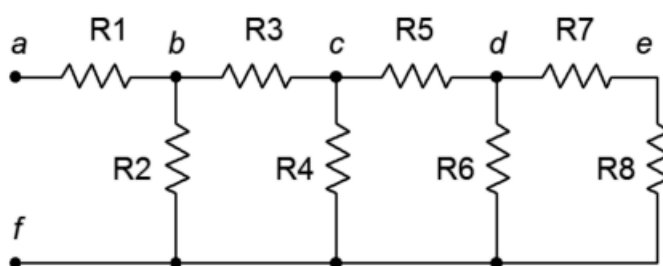- **Ladders:** A ladder is a unique series-parallel configuration. It is arranged in a cascade of series and parallel connections.



The main thing to note is that the ladder network consists of “sections loading sections” repeatedly. By loading, we mean that this element (the load) draws off current and power from the prior section. As a result, simple two-resistor voltage dividers cannot be used.

The only proper voltage divider in this configuration is between R_7 and R_8 . The reason for this becomes apparent if we imagine determining the equivalent resistance of the network by placing an ohmmeter at terminals a and f . The ohmmeter will apply a current to node a which passes through R_1 . At node b this current splits, part going down R_2 and part continuing through R_3 . Clearly then, R_1 and R_2 are not in series as they do not see the same current. Further, the current that flows through R_3 enters node c where it splits again, part down R_4 with the remainder flowing through R_5 . Thus, R_3 and R_4 are not in series, either. The same sort of thing happens again at node d . This would continue for as many rungs as are on the ladder, the sole exception being the final two resistors which are in series (R_7 and R_8 here).

How then do we find the equivalent resistance of this network? We begin at the end farthest from the open terminals. We have already noted that R_7 and R_8 are in series. This pair, if treated as a single resistance, is in parallel with R_6 , or

$$R_6 \parallel (R_7 + R_8).$$

This group of three is in series with R_5 , yielding

$$R_5 + (R_6 \parallel (R_7 + R_8)).$$

This new group of four is in parallel with R_4 , yielding

$$R_4 \parallel (R_5 + (R_6 \parallel (R_7 + R_8))).$$

This group is in series with R_3 , and that new group is in turn in parallel with R_2 . Finally, that penultimate grouping is in series with R_1 . Therefore, the equivalent resistance of the network is

$$R_{eq} = R_1 + [R_2 \parallel (R_3 + [R_4 \parallel (R_5 + [R_6 \parallel (R_7 + R_8)])])].$$

Surely, it is a tad tedious to compute the value, but it is not particularly difficult. A word to the wise: if the goal is to determine the voltages at the various nodes or the myriad branch currents, it will be helpful to keep track of the equivalent resistances of the various groupings.


For example, if V_{cf} is known and the goal is to find V_{df} , the voltage-divider relationship would be

$$V_{df} = V_{cf} \frac{R_6 \parallel (R_7 + R_8)}{R_5 + (R_6 \parallel (R_7 + R_8))}.$$

Note that $\parallel$ has higher precedence than $+$ or $-$, therefore $\parallel$ is performed first, rather like multiplication when mixed with addition and subtraction.

- **Any Route Works:** To find some voltage V_{XY} , start at point X and proceed along any convenient route to Y , subtracting voltage rises (polarities of $-$ to $+$) and adding voltage drops (polarities of $+$ to $-$) along the way.
- **R-2R Ladder:** As promised earlier in the chapter, it's time to look at a ladder network. While ladders can use any resistance values desired, certain ratios turn out to be eminently practical. Of particular note is the R-2R ladder

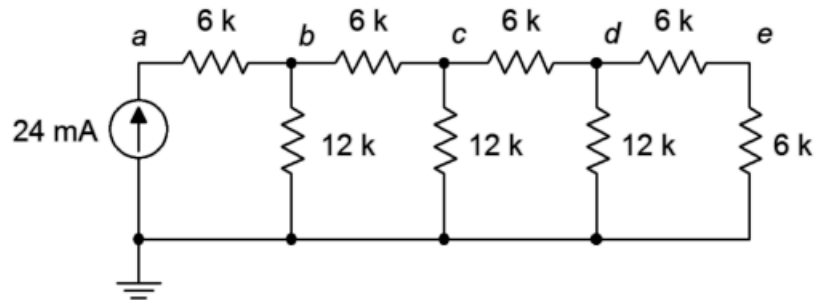In this configuration, only two different resistor values are used; some initial value and a second value of precisely twice that size



It turns out that this arrangement offers something very unique: a halving of successive node voltages and branch currents. This is extremely useful in digital to analog conversion circuits; the sort of hardware that would turn the digital bits of an MP3 or WAV file into listenable analog signals to feed loudspeakers or headphones.


Starting at the far right end, it should be obvious that the last two $6\text{ k}\Omega$ resistors comprise a 50% voltage divider, and thus V_e will half of V_d

The combination of the final three resistors works out to $12\text{ k}\Omega \parallel (6\text{ k}\Omega + 6\text{ k}\Omega)$, or $6\text{ k}\Omega$ again. Thus, the divider from c to d is also 50%. This process repeats as we move to the left, each equivalent working out to R and resulting in a 50% voltage divider. It will not matter what value is chosen for R . As long as $2R$ is used for the other set of resistors, the result will always be successive 50% voltage dividers.

- **Bridges:** A bridge is a particular series-parallel configuration consisting of two pairs of series connected elements placed in parallel.

Figure 5.21

A resistive bridge network.

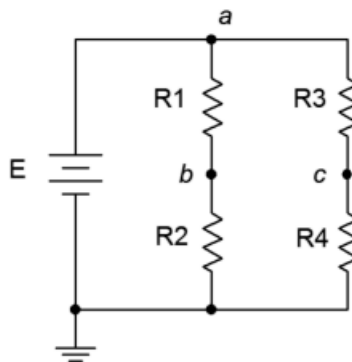

A typical use for a bridge is the measurement of some environmental quantity. There are certain resistive devices that are sensitive to environmental change. Examples include photoresistors, whose resistance is a function of light level; and thermistors, whose resistance is a function of temperature.

To understand the operation, the voltages V_b and V_c are established by the voltage dividers comprised of R_1 and R_2 ; and R_3 and R_4 , respectively. With ordinary resistors, these voltages would be unchanging and therefore V_{bc} would also be a fixed value. We shall set it up such that V_b and V_c are the same voltage, and thus V_{bc} will be zero. Now assume that we replace R_1 with a photoresistor. As the light level increases, its resistance decreases. This will cause V_b to rise which will cause V_{bc} to go positive. If the light level decreases, the resistance of R_1 will increase, forcing V_b to drop which will cause V_{bc} to go negative. The greater the change in light, the larger V_{bc} will be, and its sign indicates whether the light level has increased or decreased compared to the original set point. By simply placing some manner of voltmeter between points b and c , we can create a display that indicates light levels.

If we want to flip the sign, we would place the photoresistor in the position of R_2 instead of R_1 . Further, it is possible to increase the sensitivity by using sensors at opposite corners (e.g., R_1 and R_4), and comparative or differential measurements are possible by using both sides (e.g., R_1 with R_3).

Analysis theorems and techniques

- **Intro:** We begin by considering a more realistic model for constant voltage and constant current sources. The ideal voltage source produces a stated potential forever, and without regard to what it is connected to. The ideal current source behaves similarly; it will always produce the same current regardless of its load. These expectations are not realistic. For example, if we were to place a solid bar of copper across the terminals of a voltage source, the bar may exhibit a resistance of mere milliohms, implying an output current of thousands of amps. Similarly, if we were to disconnect a current source from any load, its effective load would be the resistance of the air between its terminals and Ohm's law would dictate an output voltage of perhaps thousands or even millions of volts. Real world sources do not behave like this.


Thus, ideal voltage and current sources cannot exist in the real world because they would theoretically produce infinite or destructive amounts of power.

- **Internal resistance (Voltage source):** A highly precise model for any voltage source or current source could be fairly complex but for general purpose work, we can greatly improve our ideal sources by simply adding a resistor to them. This resistance is referred to as the internal resistance of the source.

It is important to understand that this is not a resistor, as in an internal component that can be altered, but rather a mathematical addition to the source that better predicts how it will behave. Further, the value of this effective resistance can be deduced in a laboratory via proper measurements.

The model for a voltage source adds a resistance in series

Figure 6.1
Practical voltage source model.

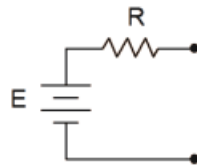

This resistance sets an upper limit on the source's current output. Even if the output terminals are shorted, the maximum current will be dictated via Ohm's law to be the source voltage divided by the internal resistance, or E/R . Obviously, this internal resistance will create some voltage divider effect with the attached load. To minimize this effect, the internal resistance should be as small as practicably possible. Thus,

"The ideal internal resistance of a voltage source is zero ohms (a short)."

Given a zero ohm internal resistance, this improved model reverts back to the original ideal source. In the case of a lab power supply, the internal resistance typically will be a small fraction of an ohm.


An ideal voltage source has zero internal resistance, meaning it maintains a completely constant terminal voltage regardless of how much current is drawn by the connected circuit. It provides a fixed voltage output at all times.

The voltage drop is then

$$V = IR = 0.$$

- **Internal resistance (Current source):** For a current source, the improved model adds a resistance in parallel

Figure 6.2
Practical current source model.

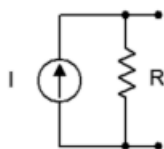

This resistance sets an upper limit on the source's voltage output. If the output terminals are opened, the maximum voltage will no longer produce a huge voltage. Instead, it is dictated by Ohm's law to be the source current times the internal resistance, or IR . This internal resistance will create some current divider effect with the attached load. To minimize this effect, the internal resistance should be as large as practicably possible. Thus,

"The ideal internal resistance of a current source is infinite ohms. "

Given an infinite ohm internal resistance (i.e., an open), this improved model reverts back to the original ideal source. From here on, whenever we deal with practical voltage and current sources, we understand that these sources have some associated internal resistance, even if they're not shown explicitly in a schematic diagram. Further, whenever we talk about ideal sources, we simply use a short for the internal resistance of a voltage source and an open for the internal resistance of a current source.

An ideal current source has infinite internal resistance, meaning it delivers a completely constant current regardless of the voltage across its terminals.

When you connect an external load (

$$R_{load}$$

):

- The total current splits into two paths: some goes through

$$R_{internal}$$

(bleed current), and the rest goes to your load.

- Because they are in parallel, both paths experience the exact same voltage (V)

Since

$$I_{\text{internal}} = \frac{V}{\infty} = 0,$$

there is no internal current bleed.

- **Open load:** An open load in a circuit is a condition where the intended device or component (the "load") is disconnected, broken, or missing, creating a break in the electrical pathway that stops current from flowing

Because the conductive path is incomplete, the electrical current drops to zero amperes ($I \approx 0$).

The gap or break acts as an extremely high (effectively infinite) resistance barrier.

While current cannot flow, the full source voltage can still be measured across the break or the terminals where the load should be

To continue, if we look at the open load case, for the voltage source the load current would be zero and the load voltage would be the entire source voltage of E . For the current source, the load would also see no current and its voltage would be the voltage appearing across its internal resistance which is R times the current E/R , or just E . Thus, the two behave identically at the load limits.

- **Source Equivalences:** For any simple voltage source consisting of an ideal voltage source with a series internal resistance, an equivalent current source may be created. Similarly, for any simple current source consisting of an ideal current source with a parallel internal resistance, an equivalent voltage source may be created. By "equivalent", we mean the load currents must be identical for both circuits given any value of load resistance. (Note that if the currents are the same then the voltages must also be the same due to Ohm's Law.)

Given a voltage source, the maximum current is developed when the load is shorted producing a current of E/R . Under that same load condition, all of the current from the current source version must be flowing through the load. Therefore, the value of the equivalent current source must be the maximum current of E/R . It would be nonsensical to use a current source that was larger or smaller than this value.

To continue, if we look at the open load case, for the voltage source the load current would be zero and the load voltage would be the entire source voltage of E . For the current source, the load would also see no current and its voltage would be the voltage appearing across its internal resistance which is R times the current E/R , or just E . Thus, the two behave identically at the load limits.

Similarly, if we start with a current source, an open load produces the maximum load voltage of IR . Therefore, the equivalent voltage source must have a value of IR . For the current source, a shorted load would produce a load current equal to the source value, or I . The voltage source version would produce a current of E/R , where the value of E was just found to be equal to IR , and thus the load current would be IR/R , or just I . Once again, the two versions behave identically at the load limits


To summarize the process of source conversion:

- The internal resistance will be the same for both versions.
- If converting from a voltage source to a current source, the value of the current source will be the maximum current available from the voltage source (shorted load case), and is equal to E/R .
- If converting from a current source to a voltage source, the value of the voltage source will be the maximum voltage available from the current source (opened load case), and is equal to IR .

If a multi-source is being converted (i.e., voltage sources in series or current sources in parallel), first combine the sources to arrive at the simplest source and then do the conversion. Do not convert the sources first and then combine them as you will wind up with series-parallel configurations rather than simple sources.

Judicious use of source conversions can sometimes simplify multi-source circuits by allowing converted sources to be combined, resulting in a single source


Now, consider

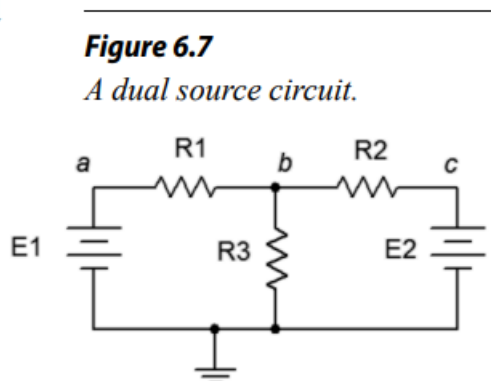


This circuit is unlike any circuit we have seen so far. Although we have analyzed circuits using multiple voltage sources, they have always been in a simple series loop. As such, their voltages may be added together to find a single equivalent voltage source. Such is not the case here. In this circuit the voltage sources are part of a series-parallel network and thus their potentials cannot be merely added. In fact, there are no further simplifications to be performed on this circuit using basic series-parallel techniques. We appear to be stuck.

But we're not. This circuit can be simplified into a straight all-parallel network through the use of source conversions. The E_1 , R_1 combo can be converted into one current source while the E_2 , R_2 combo can be converted into a second source. Once these are converted, the resulting circuit will consist of two current sources and three resistors, all in parallel

Consider

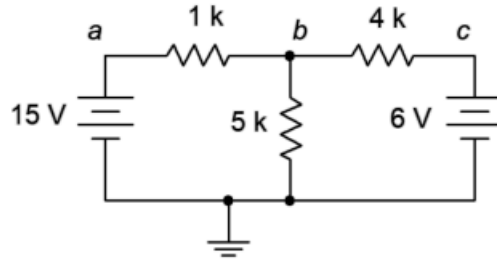

The converted circuit is then

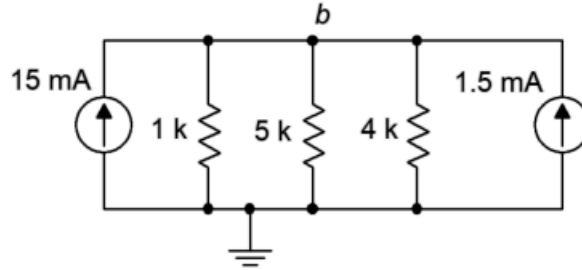

The equivalent resistance is

$$V_{EQ} = 1000 || 4000 || 5000 = 689.7\Omega.$$

Since the total current is $15 + 1.5 = 16.5\text{mA}$,

$$V_b = 0.0165(689.7) = 11.38\text{V}.$$

We can now take this voltage and apply it back to the original (unconverted) circuit. With this potential known, it is relatively easy to determine the other currents and voltages using KVL and Ohm's law.

Looking at the $1\text{k}\Omega$ resistor, the voltage across it is

$$15\text{V} - 11.38\text{V} = 3.62\text{V}.$$

Therefore, the current through it is

$$I_1 = \frac{3.62\text{V}}{1\text{k}\Omega} = 3.62\text{mA}.$$

Similarly, the voltage across the $4\text{k}\Omega$ resistor is

$$11.38\text{V} - 6\text{V} = 5.38\text{V},$$

which yields a current of

$$I_2 = \frac{5.38\text{V}}{4\text{k}\Omega} = 1.345\text{mA}.$$

Both currents flow from left to right. The third current, which flows downward through the $5\text{k}\Omega$ resistor, is

$$I_3 = \frac{11.38\text{V}}{5\text{k}\Omega} = 2.276\text{mA}.$$

According to KCL, the current entering node b must equal the total current leaving it. The entering current is 3.62mA , while the sum of the exiting currents is

$$I_2 + I_3 = 1.345\text{mA} + 2.276\text{mA} = 3.621\text{mA} \approx 3.62\text{mA}.$$

Therefore, KCL is satisfied within the rounding precision of the calculated values.

Note: In the equivalent circuit, nodes a and c disappeared. This brings up an important point. Equivalent circuits are equivalent in terms that the items connected to the equivalent behave the same way as they do with the original circuit. That does not mean that the items within the equivalent see the same current or voltage. We do not expect the voltage across the $1\text{ k}\Omega$ or $4\text{ k}\Omega$ resistors in the converted version to be the same as those in the original version.

- **Linear and bilateral circuits:** A linear circuit has an output that is directly proportional to its input, while a bilateral circuit allows current to flow and behave the same way in either direction
- **Linear circuits:** A circuit where values like resistance, inductance, and capacitance stay constant and do not change when voltage or current changes. They follow Ohm's law and obey the principle of superposition
- **Bilateral circuits:** A network or circuit whose properties and current-voltage behavior are identical regardless of the direction of the current. Reversing the voltage polarity reverses the current by the exact same magnitude, meaning the circuit is bidirectional.
- **Recall multiple voltage sources:** A voltage source acts like a pump for electrical charge, with a positive terminal pushing current out one way and a negative terminal pulling it back

When you connect the positive terminal of one battery to the negative terminal of another (+ to -), both sources pump charge in the same direction. Their efforts combine, so you add their voltages


When you connect opposing terminals together (+ to + or - to -), the two sources try to force current in opposite directions. One source tries to raise the potential while the other tries to lower it.

- **Short:** A short means a direct connection with zero ohms of resistance between two points.
- **Open:** An open circuit is an incomplete electrical path where the connection is broken, resulting in infinite resistance and zero current flow.
- **Superposition Theorem:** The superposition principle states that the total voltage or current at any point in a linear circuit with multiple independent sources is the algebraic sum of the individual voltages or currents produced by each source acting alone

Superposition allows the analysis of multi-source series-parallel circuits. Superposition can only be applied to networks that are linear and bilateral. Further, it cannot be used to find values for non-linear functions, such as power, directly. Fortunately, if the circuit contains nothing but resistors, and ordinary voltage sources and current sources, the circuit will be a linear bilateral network. Also, although power is a square law function (i.e., it is proportional to the square of voltage or current), it can be computed from the resulting voltage or current values so this presents no limits to analysis.

The basic idea is to determine the contribution of each source by itself, and then adding the results to get the final answer(s). Consider

Figure 6.10
A dual source circuit.

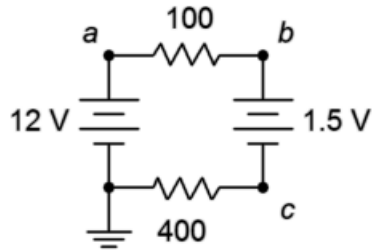


Here we have two voltage sources driving a pair of resistors. It is a basic series circuit. As the two sources are in opposition, the net voltage is 10.5 volts while the total resistance is $500\ \Omega$. This yields a circulating current of 21 mA.

From earlier work we have discovered that the ideal internal resistance of a voltage source is a short, or zero ohms. Thus, we wind up with two circuits: one with a 12 volt source that drives $100\ \Omega$, $400\ \Omega$ and a short; and a second circuit with a 1.5 volt source that drives pretty much the same thing, but with an opposing current direction.

The first circuit produces a clockwise current of $12V/500\Omega$, or 24 milliamps. Meanwhile, the second circuit produces a counterclockwise current of $1.5V/500\Omega$, or 3 mA. As these two currents oppose each other, the resulting current is $24\text{ mA} - 3\text{ mA}$, or 21 mA, the same value originally computed

- For every voltage or current source in the original circuit, create a new subcircuit. The sub-circuits will be identical to the original except that all sources other than the one under consideration will be replaced by their ideal internal resistance. This means that all remaining voltage sources will be shorted and all remaining current sources will be opened.
- Label the current directions and voltage polarities on each of the new subcircuits, as generated by the source under consideration.
- Solve each of the sub-circuits for the desired voltages and/or currents using standard series-parallel analysis techniques. Make sure to note the voltage polarities and current directions for these items.
- Add all of the contributions from each of the sub-circuits to arrive at the final values, being sure to account for current directions and voltage polarities in the process.

Reconsider

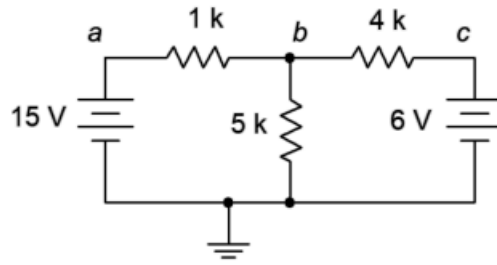

The two sub circuits are

Figure 6.12

First sub-circuit for the circuit of Figure 6.11.


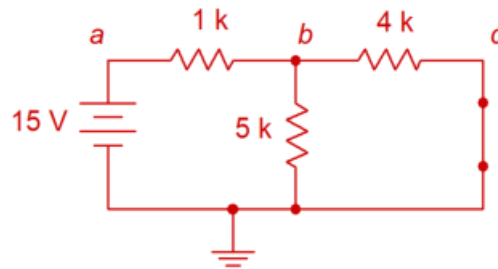


Figure 6.13

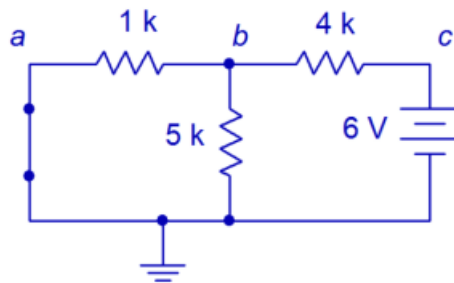Second sub-circuit for the circuit of Figure 6.11.



Solving for V_b on the first yields $V_b = 10.34V$, solving for V_b on the second yields $V_b = 1.034V$. By the superposition principle, we add both contributions. Thus, V_b in the original circuit is approximately

$$V_b \approx 11.37V.$$

If the 6V source was reversed, it would pull node b toward $-6V$. Its contribution would then be negative, since V_b in this case would be below ground.


- **Ports:** In electrical circuit theory, a port is a pair of terminals connecting a circuit or network to the outside world where the current entering one terminal must equal the current exiting the other terminal

The net current flowing into the pair of terminals must be zero. This means the current entering one terminal is equal and opposite to the current leaving the companion terminal

- **Thevenin's Theorem:** Any single port linear network can be reduced to a simple voltage source, E_{th} , in series with an internal resistance, R_{th} .

The phrase “single port network” means that the circuit is cut in such a way that only two connections exist to the remainder of the circuit (two connection points makes up one port). The remainder of the circuit may be a single component or a large multi-component sub-circuit. As there are many ways to cut a typical circuit, there are many possible Thevenin equivalents. The important thing is that there are only two connection points between the two portions of the circuit and neither point has to be ground.


Consider

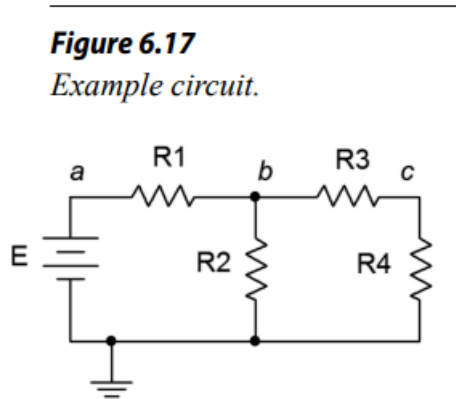


Suppose we cut the circuit immediately to the left of R_4 . That is, we will find the Thevenin equivalent that drives R_4 . The first step is to make the cut, removing the remainder of the circuit (in this case, just R_4). We then determine the open circuit output voltage. This is the maximum voltage that could appear between the cut points and is called the Thevenin voltage, E_{th} .

In a circuit such as this, basic series-parallel analysis may be used to find E_{th} . This process turns out to be quite straightforward in this particular circuit. Due to the open, no current flows through R_3 , thus no voltage is developed across R_3 , and therefore E_{th} must equal the voltage developed across R_2 which may be obtained via a voltage divider with resistor R_1 and source E .

Figure 6.18
Finding E_{th} .

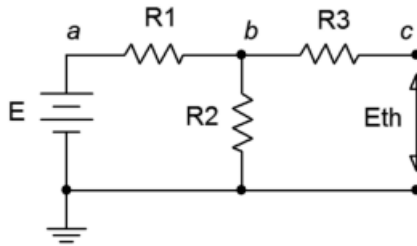

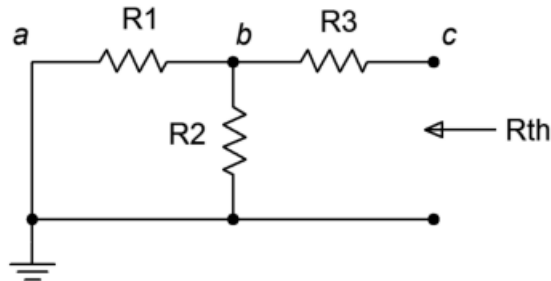
The second part is finding the Thevenin resistance, R_{th} . Beginning with the “cut” circuit, replace all sources with their ideal internal resistance (thus shorting voltage sources and opening current sources). From the perspective of the cut point, look back into the circuit and simplify by making appropriate series and parallel combinations to determine its equivalent resistance.




We find that R_1 and R_2 are in parallel, and this combination is then in series with R_3 . Thus, $R_{th} = R_3 + (R_1 || R_2)$. A common error is to determine the equivalent resistance that the source drives. Remember, everything is determined from the vantage point of the cut or port.

Thevenin equivalents are not limited to single source circuits. It is possible to find the equivalent of a network with several sources. Finding the open circuit output voltage will undoubtedly require some extra work, for example the use of superposition of source conversions. Finding the Thevenin resistance is unchanged, just remember to replace every source with its ideal internal resistance before simplifying the network.

Consider

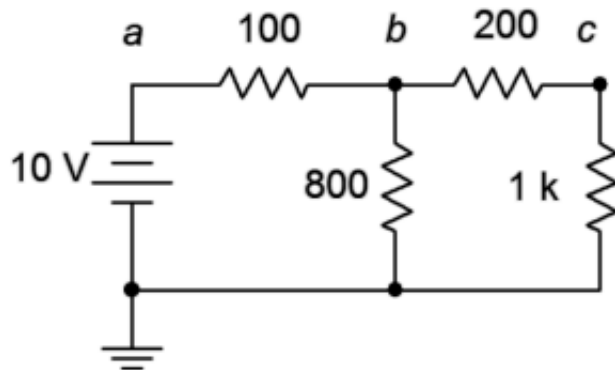

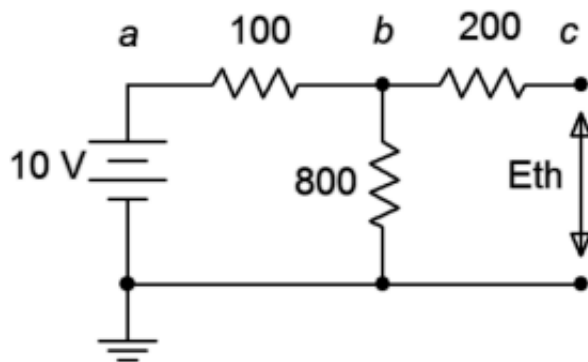Suppose we want to determine the Thevenin equivalent of the circuit driving the $1\text{k}\Omega$. Then,



Now, since there is no current passing through the 200 , we have

$$R_{EQ} = 100 + 800 = 900.$$

Thus,

$$I = \frac{10}{900} = 0.0111\text{A}.$$


Since there is no voltage drop across the 200 , E_{th} is given by the voltage at b , which is equal to the voltage drop across the 800 , or the source voltage minus the voltage drop across the 100 .

$$\begin{aligned} 10 - V_{100} &= 10 - 0.0111(100) = 8.89\text{V}, \\ 0.0111(800) &= 8.89\text{V}. \end{aligned}$$

The equivalent resistance is found by shorting the voltage source and then simplifying the circuit. We have:

$$200 + 100 || 800 = 288.89\Omega.$$

Now, we can find V_c

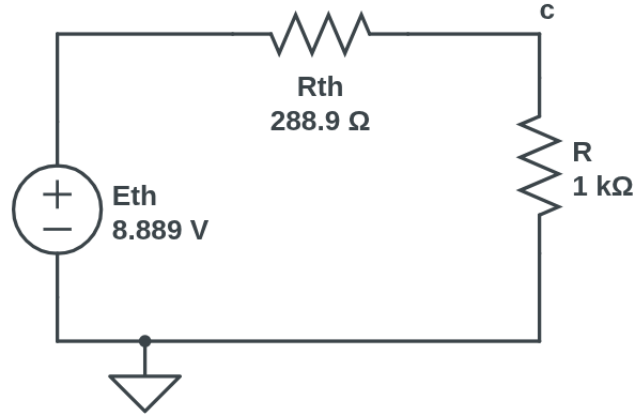

In this equivalent circuit,

$$I = \frac{8.889}{1000 + 288.89} = 0.006897 A.$$

Thus,

$$V_c = V_{1k} = 0.006987(1000) = 6.897V.$$

Now, let's analyse the original circuit. We have

$$R_{EQ} = (1000 + 200) \parallel 800 + 100 = 580\Omega.$$

Thus,

$$I = \frac{10}{580} = 0.0172 A,$$

$$V_b = 10 - 0.0172(100) = 8.276V.$$

The current through c is given by

$$I_c = I_{200} = I_{1000} = \frac{V_b}{1200} = 0.0069 A.$$

Thus,

$$V_c = 0.0069(1000) = 6.897V.$$

Notice that the voltages found at c match perfectly, while the voltage at b is only slightly off.

- **Norton's theorem:** In a nutshell, Norton's theorem is the current source version of Thevenin's theorem.

That is, a single port DC network can be reduced to a single current source, I_N , with parallel internal resistance, R_N .

replace all sources with their ideal internal resistance and then perform appropriate series and parallel combinations to reduce this to a single resistance value. Consequently, the Norton and Thevenin resistance values are identical, $R_N = R_{th}$. Second, instead of finding the open circuit output voltage, we find the short circuit output current. This is the Norton current. Instead of thinking in terms of a voltmeter at the opened load, we think in terms of connecting a shorting ammeter across the load. Either way, we're looking for the maximum value that can be obtained.

Perhaps the most useful thing to remember here is that if we can create a Thevenin equivalent for a network then it must be possible to create a Norton equivalent. Indeed, once a Thevenin equivalent is found, a source conversion can be performed on it to yield the Norton equivalent!

- **Normalized source:** Consider a source voltage E with internal resistance R_i connected in series to load resistor R . Suppose we wanted to normalize such that $E = R_i = 1$.

Define

$$E_{\text{base}} = E, \quad R_{\text{base}} = R_i.$$

Define normalized quantities by dividing each value by its corresponding base

$$e = \frac{E}{E_{\text{base}}} = 1, \quad r_i = \frac{R_i}{R_{\text{base}}} = 1.$$

The normalized load resistance becomes

$$r = \frac{R}{R_i}.$$

Normalization does not physically change E or R_i ; it expresses the circuit using E volts and R_i ohms as the chosen units.

- **Base:** A base is a chosen reference value used to express a physical quantity as a dimensionless ratio.

For any quantity X ,


$$X_{\text{normalized}} = \frac{X_{\text{actual}}}{X_{\text{base}}}.$$

To recover an actual quantity, multiply its normalized value by its base

- **Maximum Power Transfer Theorem:** Given a simple voltage source with internal resistance, a useful question to ask is “What value of load resistance will yield the maximum amount of power in the load?” While it is not true that maximizing load power is a goal of all circuit designs, it is a goal of a portion of them and thus worth a closer look.

Figure 6.28

Defining maximum power transfer.

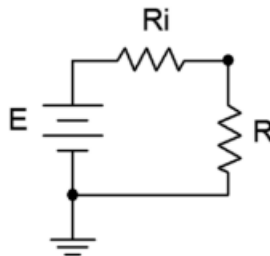

We have source E , source internal resistance R_i and load resistance R .

We would like to describe the load power in terms of the load resistance. To make the job easier, we may normalize the voltage source E to 1 volt and the source resistance R_i to 1 Ohm. By doing this, R also becomes a normalized value, that is, it no longer represents a simple resistance value but rather represents a ratio in comparison to R_i . In this way the analysis will work for any set of source values. Note that the value of E will equally scale the power in both R_i and R , so a precise value is not needed, and thus, we may as well chose 1 volt for convenience.

Note that

$$P = I^2 R, \quad I = \frac{E}{R_i + R} = \frac{1}{1 + R}.$$

Hence,

$$P = \left(\frac{1}{1 + r} \right)^2 R = \frac{R}{R^2 + 2R + 1}.$$

We now have an equation that describes the load power in terms of the load resistance. Notice that if $R = 0$ or $R = \infty$ (shorted and open case) the power is zero.


While shorting the load will yield the maximum load current, it will also yield zero load voltage and thus no power. Similarly, opening the load will yield maximum load voltage but it will also yield zero load current, and again, no load power

Its easy to see that maximum power will be achieved when $R = 1$. Thus,


"Maximum load power will be achieved when the load resistance is equal to the internal resistance of the driving source. "

While matching the resistance produces the maximum load power, it does not produce maximum load current or maximum load voltage. In fact, this condition produces a load voltage and a load current that are half of their maximums. Their product, however, is at the maximum. Further, efficiency at maximum load power is only 50% (i.e., only half of all generated power goes to the load with the other half being wasted internally). Values of R greater than R_i will achieve higher efficiency but at reduced load power. Sometimes we favor efficiency over maximal load power.

- **Delta-Y Conversions:** Certain component configurations, such as bridged networks, cannot be reduced to a single resistance using basic series-parallel conversion techniques. One method for simplification involves converting sections into more convenient forms. The configurations in question are three-point networks containing three resistors. Due to the manner in which they drawn, they are referred to as delta networks and Y networks

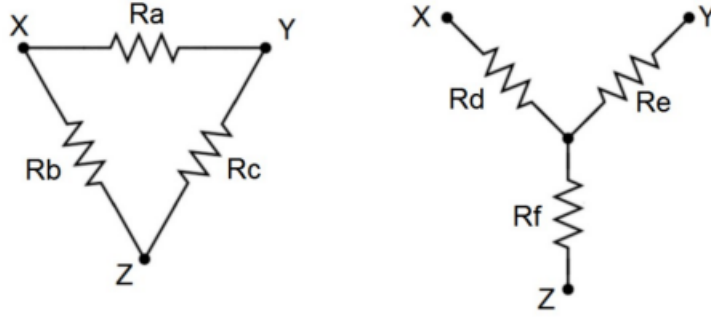

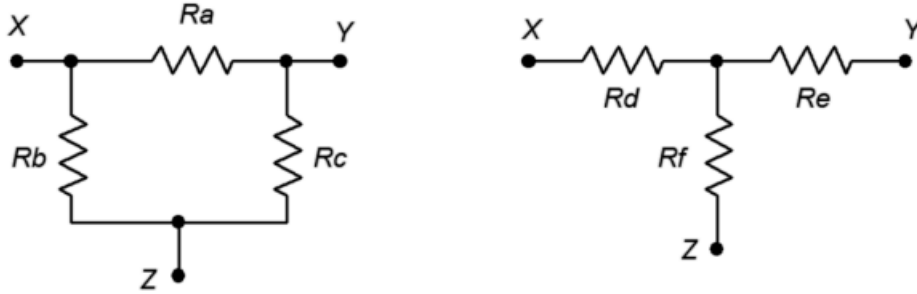Alternately, if they are slightly redrawn they are known as pi networks and T networks



It is possible to convert back and forth between delta and Y networks. That is, for every delta network, there exists a Y network such that the resistances seen between the X , Y and Z terminals are identical, and vice versa. Consequently, one configuration can replace another in order to simplify a larger circuit.

- **Δ - Y conversions:** A true equivalent circuit would present the same resistance between any two terminals as the original circuit. Consider the unloaded case. The equivalent resistances seen between each pair of terminals for the delta and Y respectively are

$$\begin{aligned} R_{XY} &= R_a || (R_b + R_c) = R_d + R_e \\ R_{XZ} &= R_b || (R_a + R_c) = R_d + R_f \\ R_{ZY} &= R_c || (R_b + R_a) = R_e + R_f. \end{aligned}$$

Assuming we have the delta and are looking for the Y equivalent, note that we have three equations with three unknowns (R_d , R_e and R_f). Thus, they can be solved using a term elimination process.

If we subtract the third equation from the first, we eliminate the second resistance (R_e) and arrive at a difference between the first and third unknown resistances ($R_d - R_f$). This quantity can then be added to the second to eliminate the third resistance (R_f), leaving just the first unknown resistance (R_d).

$$\begin{aligned} (R_d + R_e) - (R_e + R_f) &= R_d - R_f = (R_a || (R_b + R_c)) - (R_b || (R_a + R_c)), \\ (R_d + R_f) + (R_d - R_f) &= 2R_d = R_b || (R_a + R_c) + R_a || (R_b + R_c) - R_c || (R_a + R_b). \end{aligned}$$

Hence,

$$2R_d = R_b|(R_a + R_c) + R_a|(R_b + R_c) - R_c|(R_a + R_b).$$

After simplifying,

$$R_d = \frac{R_a R_b}{R_a + R_b + R_c}.$$

Similarly,

$$R_e = \frac{R_a R_c}{R_a + R_b + R_c},$$

$$R_f = \frac{R_b R_c}{R_a + R_b + R_c}.$$

- **$Y - \Delta$ conversion:** First, observe that

$$\frac{R_d}{R_e} = \frac{R_b}{R_c}.$$

Thus,

$$R_b = \frac{R_c R_d}{R_e}.$$

Similarly,

$$R_a = \frac{R_d R_c}{R_f},$$

$$R_c = \frac{R_a R_f}{R_d}.$$

Now, we can plug the expressions for R_a and R_b into

$$R_d = \frac{R_a R_b}{R_a + R_b + R_c}.$$

Thus,

$$R_d = \frac{\frac{R_d^2 R_c^2}{R_f R_e}}{\frac{R_d R_c}{R_f} + \frac{R_d R_c}{R_e} + R_c}.$$

Yielding

$$R_c = \frac{R_d R_e + R_d R_f + R_e R_f}{R_e}.$$

Now, substitute this into

$$R_b = \frac{R_c R_d}{R_e}$$

and

$$R_a = \frac{R_c R_d}{R_f}.$$

Hence,

$$\begin{aligned}R_a &= \frac{R_d R_e + R_e R_f + R_d R_f}{R_f} \\R_b &= \frac{R_d R_e + R_e R_f + R_d R_f}{R_e} \\R_c &= \frac{R_d R_e + R_e R_f + R_d R_f}{R_d}.\end{aligned}$$


If three identical resistors are used, the values of the delta equivalent will all be three times that value, the inverse of the situation when converting from delta to Y

Nodal and Mesh Analysis, Dependent Sources

- **Dependent sources:** Current and voltage sources whose value is not fixed to some particular value, but rather is dependent on some other current or voltage in the circuit.
- **Nodal and mesh analysis:** Nodal analysis and mesh analysis are two systematic methods used to solve for unknown voltages and currents in DC circuits.
- **Nodal analysis:** Nodal analysis is a technique that can be applied to virtually any circuit. In general use, it might be considered a universal solution technique as there are no practical circuit configurations that it cannot handle. Nodal analysis relies on the application of Kirchhoff's current law to create a series of node equations that can be solved for node voltages. These equations are based on Ohm's law and will be of the form $I = V/R$

Once the node voltages are obtained, finding any branch currents or component powers becomes an almost trivial exercise. We will examine two variations; a general version that can be used with both voltage and current sources, and a second somewhat quicker version that can be used with circuits only driven by current sources.

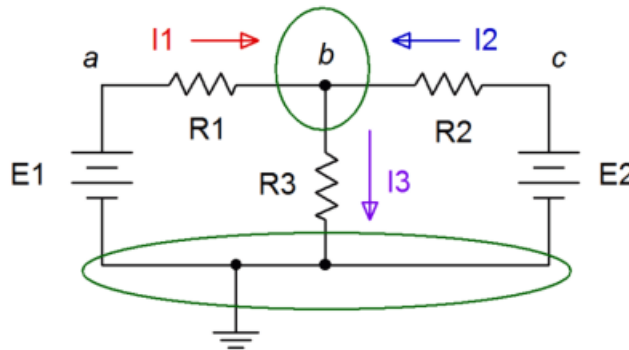- **Nodal analysis, general method:** Consider



We begin by labeling connection nodes and assigning current directions. We are particularly interested in **current junctions**, that is, places where currents can combine or split. These are also known as **summing nodes** and are circled in green on the figure. The current directions are chosen arbitrarily and may be the opposite of reality. This is not a problem. If we assign directions that are wrong, the resulting directions will ultimately show up reversed but the computed node voltages will be just fine.

One node is chosen as the reference. This is the point to which all other node voltages will be measured against. Typically, the reference node is ground, although it does not have to be.

We now write a current summation equation for each summing node, except for the reference node. In this circuit there is only one node where currents combine (other than ground) and that's node *b*. Points *a* and *c* are places where components connect,

but they are not summing nodes, so we can ignore them for now. Using KCL on node b we can say:

$$I_1 + I_2 = I_3.$$

Next, we describe these currents in terms of the node voltages and associated components via Ohm's law. For example, I_3 is the node b voltage divided by R_3 while I_1 is the voltage across R_1 divided by R_1 . This voltage is $V_a - V_b$. Therefore


$$\frac{V_a - V_b}{R_1} + \frac{V_c - V_b}{R_2} = \frac{V_b}{R_3}.$$

With $V_a = E_1$, and $V_c = E_2$ and some algebra, we have

$$\left(\frac{1}{R_1}\right) E_1 + \left(\frac{1}{R_2}\right) E_2 = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) V_b.$$

Notice that we have a series of products of conductances and voltages. All quantities are known except for V_b and thus it is easily found with a little more algebra.

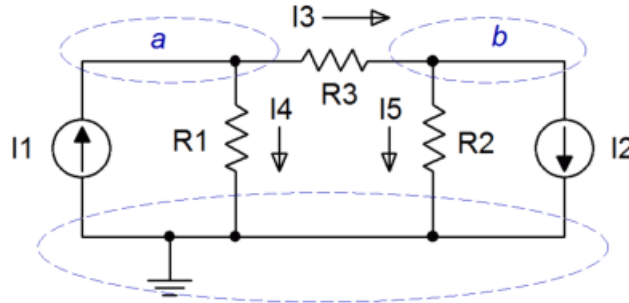For current sources, a more direct approach is possible. We start as before, identifying nodes and labeling currents.



We then write current summation equations at each node (except for ground). We consider currents entering a node as positive, and exiting as negative.

$$\text{Node a: } I_1 = I_3 + I_4$$

$$\text{Node b: } I_3 = I_2 + I_5, \text{ and rearranging in terms of the fixed source,}$$

$$\text{Node b: } -I_2 = -I_3 + I_5.$$

The currents are then described by their Ohm's law equivalents:

$$\text{Node a: } I_1 = \frac{V_a - V_b}{R_3} + \frac{V_a}{R_1}$$

$$\text{Node b: } -I_2 = -\frac{V_a - V_b}{R_3} + \frac{V_b}{R_2}.$$

Hence,

$$\text{Node a: } I_1 = \left(\frac{1}{R_1} + \frac{1}{R_3}\right) V_a - \left(\frac{1}{R_3}\right) v_b$$

$$\text{Node b: } -I_2 = -\left(\frac{1}{R_3}\right) V_a + \left(\frac{1}{R_3} + \frac{1}{R_2}\right) V_b.$$

As the resistor values and currents are known, simultaneous equation solution techniques may be used to solve for the node voltages. Once again, there will be as many equations as node voltages


- **Inspection Method:** The system of equations can be obtained directly through inspection if the circuit contains no voltage sources

For the node under inspection, sum all of the current sources connected to it to obtain the current constant. The conductance term for that node will be the sum of all of the conductances connected to that node. For the other node conductances, determine the conductances between the node under inspection and these other nodes. These terms will all be negative. As a crosscheck, the set of equations produced must exhibit diagonal symmetry.

The inspection method is summarized as follows:

1. Verify that the circuit uses only current sources with resistors and no voltage sources. If voltage sources exist, they must be converted to current sources before proceeding.
2. Find all of the current summing nodes and number them. Also decide on the reference node (usually ground).
3. To generate an equation, locate the first node. This is the node of interest and the next few steps will be associated with it.
4. Sum the current sources feeding the node of interest. Entering is deemed positive while exiting is deemed negative. The sum is placed on one side of the equals sign.
5. Next, find all of the resistors connected to the node of interest and write them as a sum of conductances on the other side of the equals sign, the group being multiplied by this node's voltage (e.g., V_1).
6. Now find all of the resistors that are connected to the node of interest and to other nodes (except the ground reference). For each of these other nodes, multiply the sum of the conductances between the node of interest and this other node by this other node's voltage, and then subtract that product from the equation built so far. Once all other nodes are considered, this equation is finished.
7. Find the next node and treat this as the new node of interest.
8. Repeat steps 4 through 7 until all nodes have been treated as the node of interest. Each iteration creates a new equation. There will be as many equations as there are nodes, less the reference node. Check for diagonal symmetry and solve.

As an example, consider

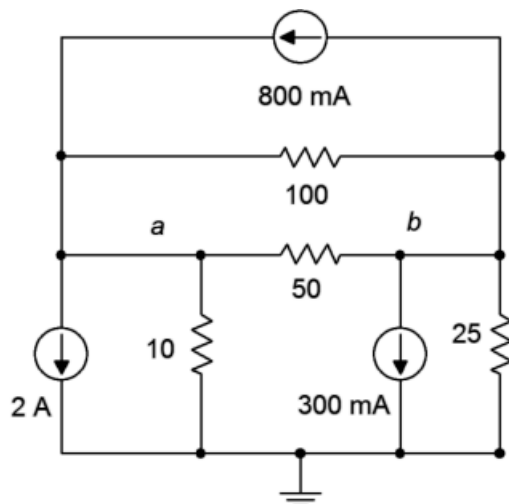

Observe the three nodes a , b and reference ground. Focus on node a . The current sources feeding this node are 800mA in, 2mA out. Thus,

$$0.8A - 2A = \dots$$

The conductances connected to node a give

$$0.8A - 2A = \left(\frac{1}{10} + \frac{1}{50} + \frac{1}{100} \right) V_a \dots$$

Now find all of the resistors that are connected to this node and to the other nodes. Multiply those resistors (expressed as conductances) by the other associated node voltages and subtract the products from the expression built so far. Repeat for all remaining nodes except the ground reference. In this example there is only one other node, node b , and thus only one iteration.

$$\begin{aligned} 0.8A - 2A &= \left(\frac{1}{10} + \frac{1}{50} + \frac{1}{100} \right) V_a - \left(\frac{1}{50} + \frac{1}{100} \right) V_b \\ &= -1.2A = 130mSV_a - 30mSV_b. \end{aligned}$$

Recall that conductance is expressed in **siemens** (S).

Now we repeat the entire process for the next equation. Node b is our new node of interest. The fixed current sources are:

$$\begin{aligned} -800mA - 300mA &= - \left(\frac{1}{50} + \frac{1}{100} \right) V_a + \left(\frac{1}{25} + \frac{1}{50} + \frac{1}{100} \right) V_b \\ &= -1.1A = -30mSV_a + 70mSV_b. \end{aligned}$$

Hence, our two equations are

$$\begin{aligned} -1.2A &= 130mSV_a - 30mSV_b \\ -1.1A &= -30mSV_a + 70mSV_b. \end{aligned}$$

So,

$$\begin{pmatrix} 0.130 & -0.030 \\ -0.030 & 0.070 \end{pmatrix} \begin{pmatrix} V_a \\ V_b \end{pmatrix} = \begin{pmatrix} -1.2 \\ -1.1 \end{pmatrix}.$$

Notice that we indeed have symmetry. Solving this system yields


$$\begin{aligned} V_a &= -14.27V, \\ V_b &= -21.83V. \end{aligned}$$

The current flowing through the 100 Ω resistor is

$$\frac{V_a - V_b}{100} = 75.6mA$$

flowing left to right.

Next, consider

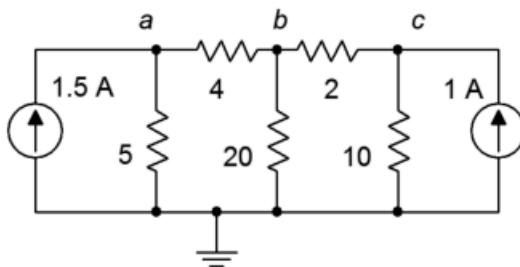

We get

$$\begin{pmatrix} 0.4 & -0.25 & 0 \\ -0.25 & 0.8 & -0.5 \\ 0 & -0.5 & 0.6 \end{pmatrix} \begin{pmatrix} V_a \\ V_b \\ V_c \end{pmatrix} = \begin{pmatrix} 1.5 \\ 0 \\ 1 \end{pmatrix}.$$

Thus,


$$V_a = 8.62V$$

$$V_b = 7.8V$$


$$V_c = 8.17V.$$

- **Converting Sources and Other Simplifications:** Given circuits with voltage sources, it may be easier to convert them to current sources and then apply the inspection technique rather than using the general approach outlined initially. There is one trap to watch out for when using source conversions: the voltage across or current through a converted component will most likely not be the same as the voltage or current in the original circuit. This is because the location of the converted component will have changed.

Consider

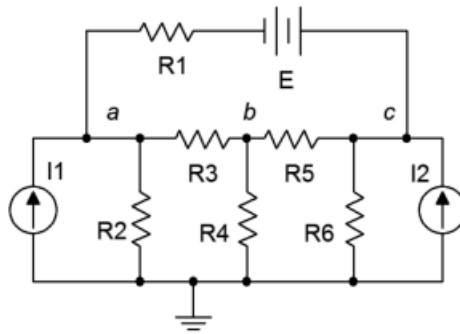

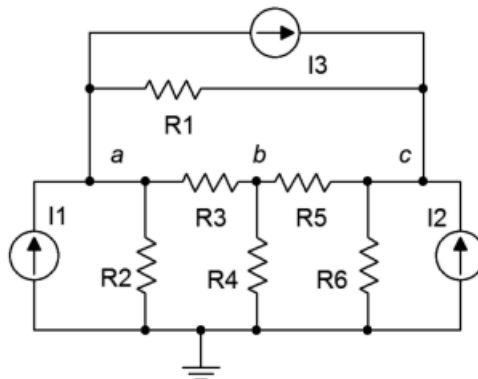could be solved using nodal analysis by converting the voltage source and the associated resistance into a current source. That is, E/R_1 would be converted into a source I_3 with a parallel resistor R_1 .




In the converted circuit, although R_1 still connects to node a , the other end no longer connects to the voltage source. Rather, the right side now connects to node c . Therefore, the voltage drop across R_1 in the converted circuit is not likely to equal the voltage drop seen across R_1 in the original circuit (unless E was 0 volts).

In the converted circuit, nodes a and c have not changed from the original, so the original voltage across R_1 can be determined via V_a , V_c and E in the original circuit

If a circuit uses voltage sources exclusively, or even a very large proportion of voltage sources, an alternate technique called mesh analysis may be a better choice than using numerous conversions.

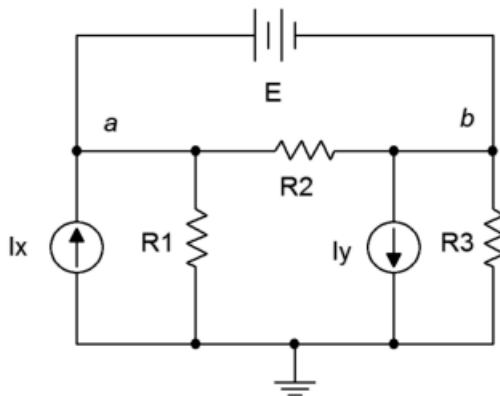- **Reduction:** A final item to consider is to simplify resistor networks in order to reduce the number of nodes. Fewer nodes means fewer equations and a quicker solution.
- **Supernode:** Consider



On occasion you may come across a circuit like this, a voltage source without a series resistance. Without that resistance, it becomes impossible to create an expression for the current passing through the source using the general method, and impossible to convert the voltage source into a current source in order to use the inspection method.


One possible way out of this quandary is to simply add a very small resistor in series with it so that a source conversion is possible. The resistor in question would have to be much smaller than any surrounding resistors in order to have minimal impact on the results. A reduction by two orders of magnitude would generally yield a variation smaller than that produced by resistor tolerances in all but high precision circuits. The other way out is to use a **supernode**.

A supernode is, in effect, the combination of two nodes. It relies on a simple observation. Notice that the path of the voltage source produces identical currents flowing into and out of nodes a and b

As a consequence, if we treat the two nodes as one big node, then when we write a KCL summation, these two terms will cancel.

Note: For a two-terminal voltage source, the current leaving the positive terminal has the same magnitude as the current entering the negative terminal. The current may split into several paths throughout the external circuit, but all those branch currents eventually recombine before returning to the negative terminal. Charge cannot continuously accumulate inside the source or circuit.

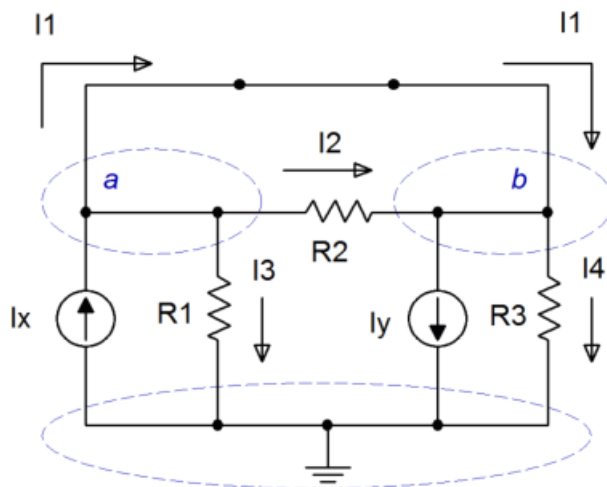This describes a voltage source **delivering power**. If current instead enters the positive terminal and leaves the negative terminal, the source is **absorbing power**, as when a battery is being charged.



In this version we have replaced the voltage source with its ideal internal resistance, a short. We have also labeled the two nodes of interest, a and b , and labeled the currents, drawn with convenient directions

Due to the shorted voltage source, nodes a and b are now the same node. Consider the currents entering and exiting this combined or “super” node. On the left side (formerly node a) we see a constant current I_x entering while I_1 , I_2 and I_3 are exiting. On the right side (formerly node b) we see I_y exiting along with I_4 , and entering we see I_1 and I_2 . Now let’s set up the entering currents on the left side of the equals sign with the exiting currents on the right:


$$\sum I_{\text{in}} = I_x + I_1 + I_2 = \sum I_{\text{out}} = I_y + I_1 + I_2 + I_3 + I_4.$$

Thus,

$$I_x - I_y = I_3 + I_4 = \frac{1}{R_1}V_a + \frac{1}{R_3}V_b.$$

We also know that $V_a - V_b = E$ from the original circuit. Assuming all sources and resistors are known, that makes two equations with two unknowns, solvable using simultaneous equation techniques.

Consider

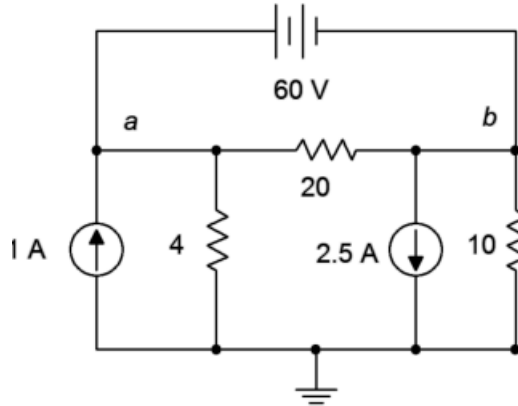

The KCL equation for node a is

$$1 + I_E - \frac{V_a - V_b}{20} - \frac{V_a}{4} = 0.$$

The KCL equation for node b is

$$-2.5 + \frac{V_a - V_b}{20} - I_E - \frac{V_b}{10} = 0.$$

Adding these two yields

$$-\frac{V_a}{4} - 1.5 - \frac{V_b}{10} = 0.$$

Hence,

$$\frac{V_a}{4} + \frac{V_b}{10} = -1.5.$$

The second equation is $V_a - V_b = 60$. Thus,

$$\begin{pmatrix} 0.25 & 0.1 \\ 1 & -1 \end{pmatrix} \begin{pmatrix} V_a \\ V_b \end{pmatrix} = \begin{pmatrix} -1.5 \\ 60 \end{pmatrix}.$$

Therefore,

$$\begin{aligned} V_a &= 12.857V \\ V_b &= -47.143V. \end{aligned}$$

- **Planar circuit:** A planar circuit is an electrical circuit that can be drawn on a flat, two-dimensional surface without any of its wires or branches crossing each other. The defining feature is that a crossing-free drawing can exist

In essence, these circuits can be drawn so that they appear like a series of window panes.

- **Branch current and mesh current:** Branch currents are the actual, physical currents flowing through individual components in a circuit, while mesh currents are mathematical loop currents used to simplify circuit analysis

A branch current is a hypothetical circulating current assigned to a closed loop or "window" of a planar circuit. It is purely conceptual; shared elements carry a net combination of adjacent mesh currents rather than a single standalone mesh current


- **Mesh analysis:** In some respects mesh analysis is a mirror of nodal analysis. While nodal analysis leverages KCL to create a series of node equations that are used to solve for node voltages, mesh analysis uses KVL to create a series of loop equations that can be solved for mesh currents.

While branch currents represent the current flowing through a particular component, mesh currents combine to create branch currents. That is, the current through any particular component may be an individual mesh current or a combination of two mesh currents.

Circuits using complex series-parallel arrangement with multiple voltage and/or current sources may be solved using this technique. It is, however, limited to planar circuits

Non-planar circuits may be 3D in appearance and in such a circuit it becomes impossible to define the loop equations as any given component might have more than two meshing currents.

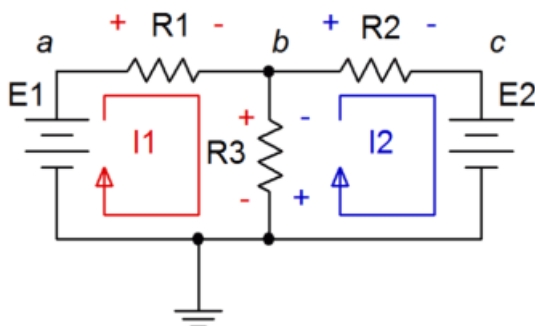- **General method:** We begin by designating a series of loops. These loops should be minimal in size and cover all components at least once. By convention, the loops are drawn clockwise. There is nothing magic about them being clockwise, it is just a matter of consistency. The current path along a loop is referred to as a mesh current.



we have two loops, and thus, two mesh currents, I_1 and I_2 . Note that all components exist in at least one loop (and sometimes in more than one loop, like R_3). Depending on circuit values, one or more of these loop's directions may in fact be opposite of reality. This is not a problem. If this is the case, the currents will show up as negative values, and thus we know that they're really flowing counter-clockwise.

$$\text{Loop 1: } E_1 = \text{voltage across } R_1 + \text{voltage across } R_3$$

$$\text{Loop 2: } -E_2 = \text{voltage across } R_2 + \text{voltage across } R_3.$$

E_2 is negative as I_2 is drawn flowing out of its negative terminal. If we choose downward as the positive reference direction, then I_1 is positive and I_2 is negative. Using Ohm's law:

$$\begin{aligned} E_1 &= I_1 R_1 + (I_1 - I_2) R_3 \\ -E_2 &= I_2 R_2 + (I_2 - I_1) R_3. \end{aligned}$$

For the second loop, we take upward current to be positive.

- For loop 1, you traverse R_3 downward, so the current in that direction is

$$I_{R_3,\downarrow} = I_1 - I_2.$$

- For loop 2, you traverse R_3 upward, so the current in that direction is

$$I_{R_3,\uparrow} = I_2 - I_1.$$

These are the same physical current expressed using opposite reference directions:

$$I_{R_3,\uparrow} = -I_{R_3,\downarrow}.$$


Therefore, it is valid to use downward as positive while writing loop 1 and upward as positive while writing loop 2. You simply must remain consistent within each equation.

We have

$$\begin{aligned} E_1 &= (R_1 + R_3)I_1 - R_3I_2 \\ -E_2 &= R_3I_1 + (R_2 + R_3)I_2. \end{aligned}$$

Assuming that the resistor values and source voltages are known, we have two equations with two unknowns. These can be solved for I_1 and I_2 using simultaneous equation solution techniques such as determinants or Gauss-Jordan elimination.

Consider an example

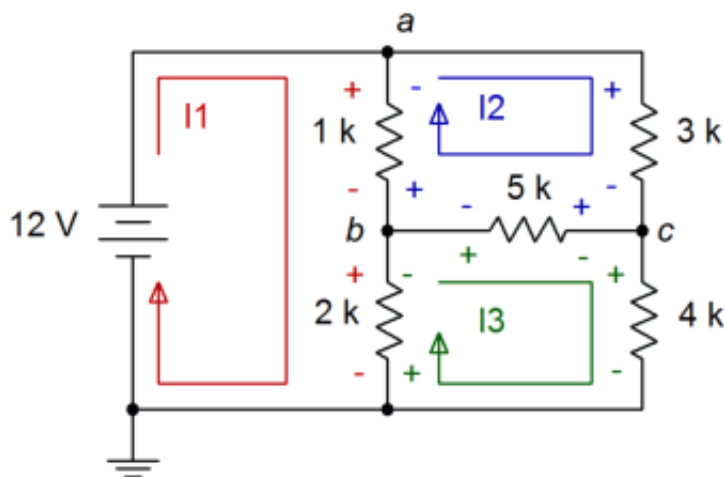

We have

$$\begin{aligned} \ell_1 : 12V &= (I_1 - I_2)1k + (I_1 - I_3)2k \\ \ell_2 : 0V &= (I_2 - I_1)1k + 3kI_2 + (I_2 - I_3)5k \\ \ell_3 : 0V &= (I_3 - I_2)5k + 4kI_3 + (I_3 - I_1)2k. \end{aligned}$$

Thus, the system is

$$1000 \begin{pmatrix} 3 & -1 & -2 \\ -1 & 9 & -5 \\ -2 & -5 & 11 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 12 \\ 0 \\ 0 \end{pmatrix}.$$

Hence,

$$I_1 = 5.729mA$$

$$I_2 = 1.626mA$$

$$I_3 = 1.781mA.$$

To find V_b , we use net current through the $2k$ resistor. Thus,

$$V_b = (I_1 - I_3)2000 = 7.8968V.$$


Similarly,

$$V_{bc} = (I_3 - I_2)5000 = 774mV.$$

- **Inspection Method:** Like nodal analysis, there is a method to generate the equations by inspection. Simply focus on one loop, which we'll call the loop under inspection, and ask the following questions: what is the total source voltage in this loop? This yields the voltage constant for the equation. Then sum all of the resistance values in the loop under inspection. This yields the coefficient for that current term. For the remaining current coefficients in this equation, sum the resistances that are in common between the loop under inspection and the other loops, respectively. These values will always be negative. Repeat this process for all loops, with each loop in turn becoming the loop under inspection. As was the case with nodal analysis, the set of equations produced must exhibit diagonal symmetry

While it is possible to extend this technique to include current sources, it is often easier and less error-prone to convert the current sources into voltage sources and continue with the direct inspection method outlined above. Either way, it is important to remember that the number of loops determines the number of equations to be solved.

Consider

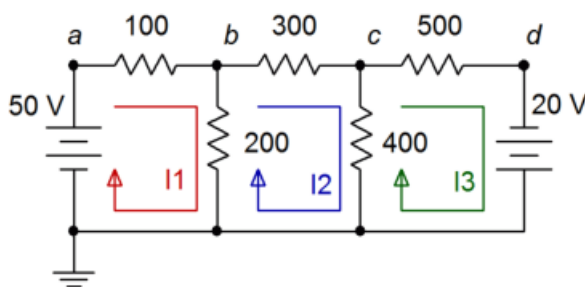

We have

$$50V = (100 + 200)I_1 - 200I_2 = 300I_1 - 200I_2$$

$$0V = (300 + 400 + 200)I_2 - 200I_1 - 400I_3 = -200I_1 + 900I_2 - 400I_3$$


$$20V = (500 + 400)I_3 - 400I_2 = 0I_1 - 400I_2 + 900I_3.$$

Thus,

$$\begin{pmatrix} 300 & -200 & 0 \\ -200 & 900 & -400 \\ 0 & -400 & 900 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix} = \begin{pmatrix} 50 \\ 0 \\ 20 \end{pmatrix}.$$


- **Supermesh:** Sometimes you may run across a current source which has no associated internal resistance

This is similar to the situation seen previously under nodal analysis where a voltage source does not have a specified internal resistance. There are two ways of solving this predicament. The first is add a very large resistance in parallel with the current source and then perform a source conversion on the pair so that the inspection method of mesh can be followed. The larger the value of this resistor, the more accuracy that is obtained. As a general rule it should be, at minimum, at least a couple of orders of magnitude larger than any surrounding resistor, and preferably larger. The second method is to use supermesh. A supermesh is a larger mesh loop that contains other mesh loops inside of it.

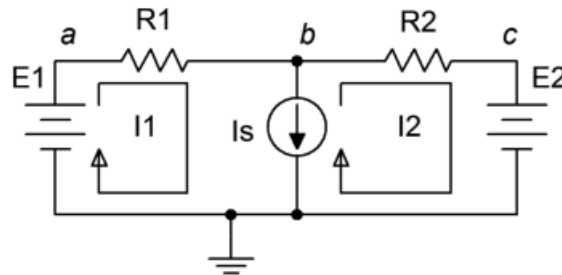

In the center we have a current source, I_s , which lacks an associated internal resistance. Two traditional mesh loops, I_1 and I_2 , are labeled as usual. The problem here is that we cannot use an Ohm's law based IR voltage drop for V_b . We have no way to express this as the voltage across I_s is an unknown. On the other hand, what we do know is that I_s must equal the combination of the traditional mesh currents I_1 and I_2 . That is, from the perspective of the first loop, $I_s = I_1 - I_2$. Remember, one or both of the mesh currents could be negative, and thus rotating counterclockwise.

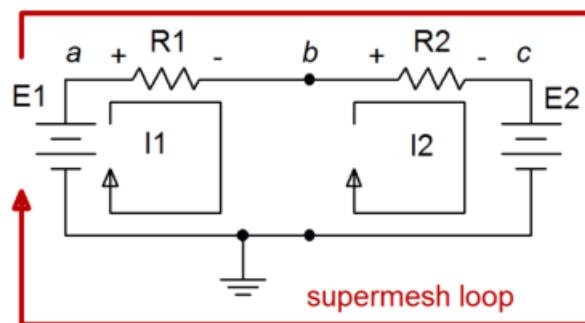At this point we invoke the idea of a supermesh loop. First, we replace the offending current source with its ideal internal resistance (an open). The supermesh loop is drawn which encompasses the original two loops.



We now perform a KVL summation around the supermesh loop, similar to what we have done previously. The difference this time is that we need to recognize that components each see one of the original mesh currents; namely I_1 or I_2 in this case.

We do not solve for a supermesh current, we simply use the supermesh to define the loop for the KVL summation

$$\sum V_{\text{rises}} = E_1 = \sum V_{\text{drops}} = V_{R_1} + V_{R_2} + E_2.$$

The voltage drops across the resistors can be expanded using Ohm's law, using the original mesh current associated with each resistor.


$$E_1 - E_2 = I_1 R_1 + I_2 R_2.$$

By inspection,


$$I_S = I_1 - I_2.$$

We now have two equations with two unknowns and can solve for I_1 and I_2 .

Consider

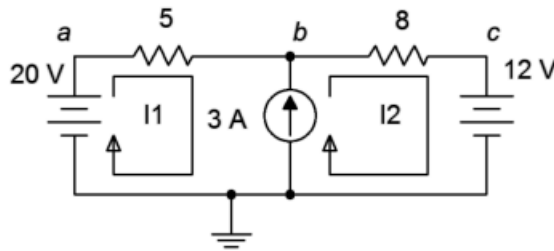

So, we have

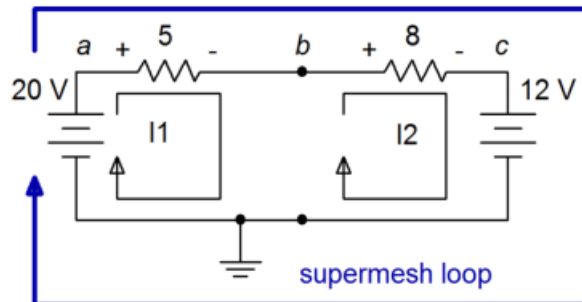

By KVL, we have

$$20 = 5I_1 + 8I_2 + 12.$$

So,

$$8 = 5I_1 + 8I_2.$$

By inspection,

$$3 = -I_1 - I_2.$$

Thus,

$$\begin{pmatrix} 5 & 8 \\ -1 & 1 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \end{pmatrix} = \begin{pmatrix} 8 \\ 3 \end{pmatrix}.$$

So,

$$I_1 = -1.231A$$

$$I_2 = 1.769A.$$

- **Dependent Sources:** A dependent source is a current or voltage source whose value is not fixed (i.e., independent) but rather which depends on some other circuit current or voltage. The general form for the value of a dependent source is


$$Y = kX$$

where X and Y are currents or voltages and k is a proportionality factor. For example, the value of a dependent voltage source may be a function of a current, so instead of the source being equal to, say, 10 volts, it could be equal to twenty times the current passing through a particular resistor, or $V = 20I$.

There are four possible dependent sources: the voltage-controlled voltage source (VCVS), the current-controlled voltage source (CCVS), the voltage-controlled current source (VCCS), and the current-controlled current source (CCCS).

The source and control parameters are the same for both the VCVS and the CCCS so k is unitless (although it may be given as volts/volt and amps/amp, respectively). For the VCCS and CCVS, k has units of amps/volt and volts/amp, respectively. These are referred to as the **transconductance** and **transresistance** of the sources with units of siemens and ohms, respectively.

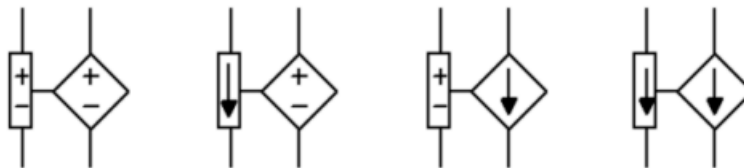The schematic symbols for dependent or controlled sources are usually drawn using a diamond. Also, there may be a secondary connection for the controlling current or voltage.




On each of these symbols, the control element is shown to the left of the source. This portion is not always drawn on a schematic. Instead, the source simply may be labeled as a function. For example,

$$V = 0.02I_x$$

where I_x is the controlling current. Dependent sources are not “off-the-shelf” items in the same way that a battery is. Rather, dependent sources usually are used to model the behavior of more complex devices. For example, a bipolar junction transistor commonly is modeled as a CCCS while a field effect transistor may be modeled as a VCCS.


Similarly, many op amp circuits are modeled as VCVS systems. Solutions for circuits using dependent sources follow along the lines of those established for independent sources (i.e., the application of Ohm’s law, KVL, KCL, etc.), however, the sources are now dependent on the remainder of the circuit which tends to complicate the analysis.

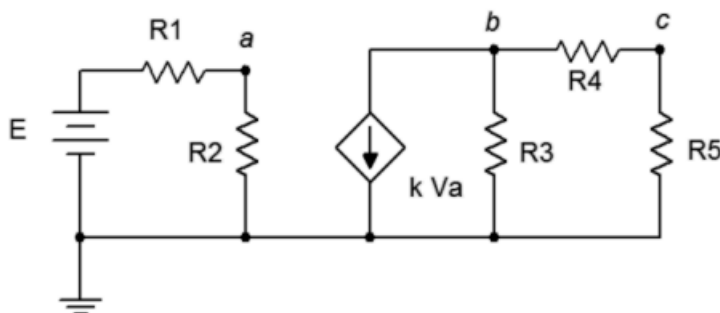- **Isolated and coupled:** In general, there are two possible configurations: isolated and coupled. A example of the isolated form is



In this configuration, the dependent source (center) does not interact with the sub-circuit on the left driven by the independent source, thus it can be analyzed as two separate circuits. Solutions for this form are relatively straightforward in that the control value for the dependent source can be computed directly. This value is then substituted into the dependent source and the analysis continues as is usual. Sometimes it is convenient if the solution for a particular voltage or current is defined in terms of the control parameter rather than as a specific value (e.g., the voltage across a particular resistor might be expressed as $8 V_A$ instead of 12 volts, where V_A is 1.5 volts).

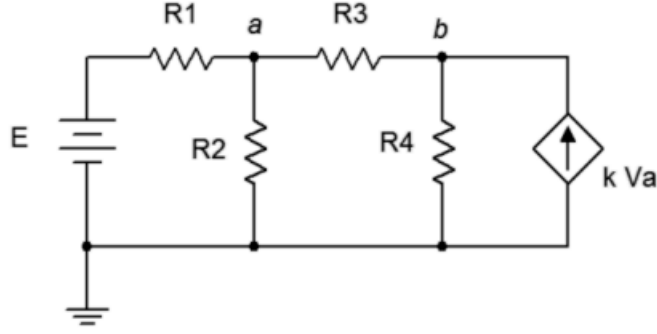The second type of circuit (coupled) is somewhat more complex in that the dependent source can affect the parameter that controls the dependent source. In other words, the dependent source(s) will contribute terms that include the controlling parameter(s), thus partly controlling itself. Some additional effort will be in order to solve these circuits.



In this example it should be obvious that the current from the dependent source can affect the voltage at node a, and it is this very voltage that in turn sets up the value of the current source. Circuits of this type can be analyzed using mesh or nodal analysis. Nodal analysis works well here and is illustrated following.

We begin by defining current directions. Assume that the currents through R_1 and R_3 are flowing into node a, the current through R_2 is flowing out of node a, and the current through R_4 is flowing out of node b. We shall number the branch currents to reflect the associated resistor.

$$\text{Node } a: I_1 + I_3 = I_2$$

$$\text{Node } b: kV_a = I_3 + I_4.$$

Notice that

$$I_1 = \frac{E - V_a}{R_1}$$

$$I_2 = \frac{V_a}{R_2}$$

$$I_3 = \frac{V_b - V_a}{R_3}$$

$$I_4 = \frac{V_b}{R_4}.$$

Thus,

$$\text{Node } a: \frac{E - V_a}{R_1} + \frac{V_b - V_a}{R_3} = \frac{V_a}{R_2}$$

$$\text{Node } b: kV_a = \frac{V_b - V_a}{R_3} + \frac{V_b}{R_4}.$$

Hence,

$$\text{Node } a: \frac{E}{R_1} - \frac{V_a}{R_1} + \frac{V_b}{R_3} - \frac{V_a}{R_3} = \frac{V_a}{R_2}$$

$$\text{Node } b: kV_a = \frac{V_b}{R_3} - \frac{V_a}{R_3} + \frac{V_b}{R_4}.$$

So,


$$\text{Node } a: \frac{E}{R_1} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) V_a - \frac{1}{R_3} V_b$$

$$\text{Node } b: 0 = - \left(k + \frac{1}{R_3} \right) V_a + \left(\frac{1}{R_3} + \frac{1}{R_4} \right) V_b.$$

Values for the resistors, k , and E normally are known, so the analysis proceeds directly.

Also, it is worth remembering that it is possible to perform source conversions on dependent sources, within limits. The same procedure is followed as for independent sources. The new source will remain a dependent source (e.g., converting VCVS to VCCS). This process is not applicable if the control parameter directly involves the internal impedance (i.e., is its voltage or current).

Consider

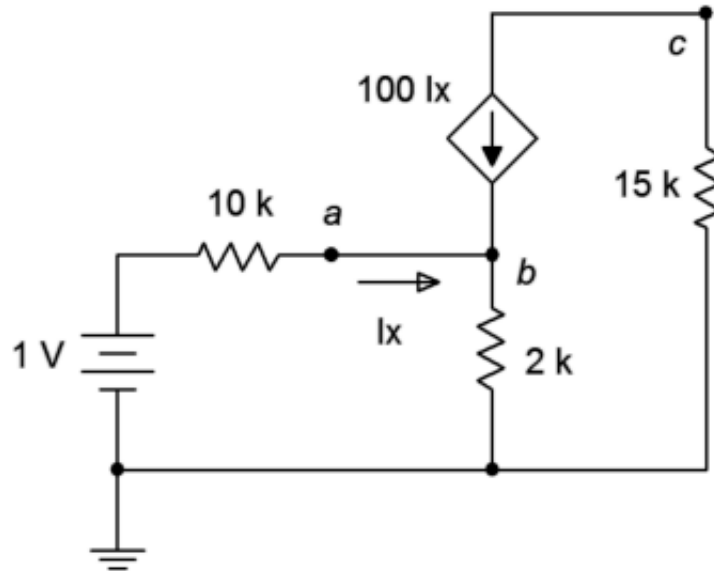

First observe that a and b refer to the same node. This CCCS would be typical of a simple model of a bipolar junction transistor (nodes a , b , and c). Ideally, the output voltage, V_c , would be equal to the input voltage (1 V) times the resistor ratio of $15\text{ k}\Omega / 2\text{ k}\Omega$ and inverted, or approximately -7.5 volts. In reality, it usually comes up a little short of this. Let's see how well this works out.

Note that

$$I_x = \frac{1V - V_b}{10k}.$$

Using KCL at node b , we have

$$I_x + 100I_x = 101I_x = 101 \frac{1 - V_b}{10000} = \frac{V_b}{2000}.$$

Thus,

$$\frac{101}{10k} = \left(\frac{1}{2k} + \frac{101}{10k} \right) V_b.$$

Hence,

$$V_b = 0.95283V.$$

For node c :

$$-\frac{V_c}{15k} = 100I_x = 100\frac{1 - V_b}{10k}.$$

So,


$$V_c = -7.0755V.$$

Capacitors

- **Intro:** Capacitors are fundamentally different from resistors in terms of both their construction and their operation. For starters, when placed in DC circuits, capacitors are not ohmic, unlike resistors. Their current-voltage characteristic does not respond to Ohm's law. Instead, their current-voltage characteristic is dynamic in nature. Further, in the ideal case, capacitors do not dissipate power. Indeed, capacitors are energy storage devices. In a way, you could imagine them to be a little like rechargeable batteries, but unlike batteries these devices could be charged or discharged in tiny fractions of a second and last for billions upon billions of cycles.

Capacitors are an integral part of modern electronic systems. They are used in AC-to-DC power supplies to help smooth and stabilize the output voltage. In audio and communications systems they are used in filters, for example to control the high and low frequency response of amplifiers and similar equipment, or for tuning purposes. Essentially, in any application that needs to smooth out a varying voltage, store electric charge or filter a signal; a capacitor is likely to be used.

- **Capacitance and Capacitors:** A capacitor is a device that stores energy. Capacitors store energy in the form of an electric field. At its most simple, a capacitor can be little more than a pair of metal plates separated by air. As this constitutes an open circuit, DC current will not flow through a capacitor. If this simple device is connected to a DC voltage source. Negative charge will build up on the bottom plate while positive charge builds up on the top plate. This process will continue until the voltage across the capacitor is equal to that of the voltage source. In the process, a certain amount of electric charge will have accumulated on the plates.

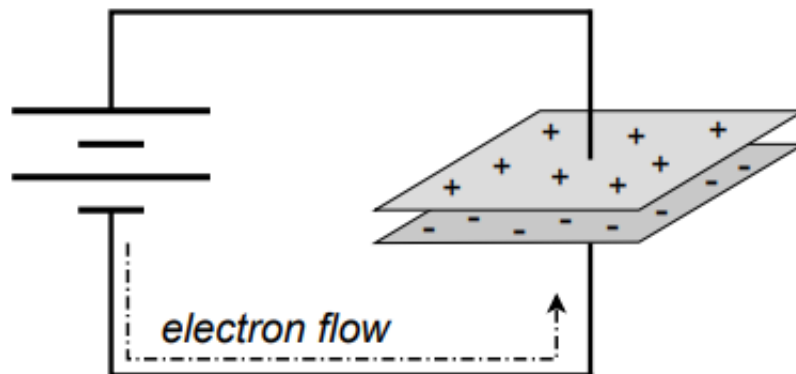

The ability of this device to store charge with regard to the voltage appearing across it is called **capacitance**. Its symbol is C and it has units of **farads (F)**.

By definition, if a total charge of 1 coulomb is associated with a potential of 1 volt across the plates, then the capacitance is 1 farad

$$1 \text{ farad} \equiv 1 \text{ coulomb} / 1 \text{ volt.}$$

That is,


$$C = \frac{Q}{V}.$$

For any given voltage, the greater the capacitance, the greater the amount of charge that can be stored. We can also see that, given a certain size capacitor, the greater the voltage, the greater the charge that is stored. These observations relate directly to the amount of energy that can be stored in a capacitor.

Unsurprisingly, the energy stored in capacitor is proportional to the capacitance. It is also proportional to the square of the voltage across the capacitor.

$$W = \frac{1}{2}CV^2.$$

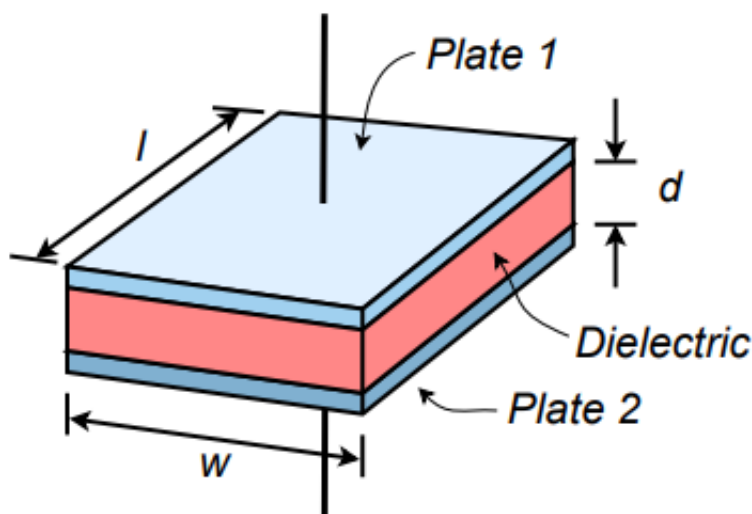The basic capacitor consists of two conducting plates separated by an insulator, or dielectric. This material can be air or made from a variety of different materials such as plastics and ceramics.




For practical capacitors, the plates may be stacked alternately or even made of foil and formed into a rolled tube. However it is constructed, the characteristics of the dielectric will play a major role in the performance of the device, as we shall see.

In general, capacitance increases directly with plate area, A , and inversely with plate separation distance, d . Further, it is also proportional to a physical characteristic of the dielectric; the **permittivity**, ϵ . Thus, capacitance is equal to:

$$C = \epsilon \frac{A}{d}.$$

- **Fringing:** It should be noted that the effective plate area is somewhat larger than the precise physical area of the plates. This is due to a phenomenon called **fringing**. Essentially, the electric field lines bulge outward at the plate edges rather than maintain uniform parallel orientation.

Figure 8.3
Capacitor electric field with fringing.

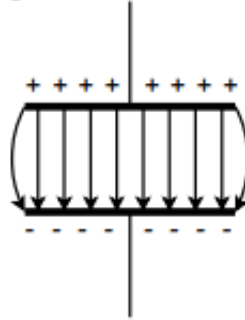

- **Efficiency:** the permittivity of the dielectric plays a major role in determining the **volumetric efficiency** of the capacitor, in other words, the amount of capacitance that can be packed into a given sized component. Some dielectrics are notably more efficient than others. To make comparisons easier, **relative permittivity** is often used, that is, the ratio of the dielectric's permittivity to that of a vacuum, ϵ_0

It might seem that choosing the dielectric with the highest permittivity would be the best choice but this is not necessarily the case. There are several other factors that go into this decision including temperature stability, leakage resistance (effective parallel resistance), ESR (equivalent series resistance) and breakdown strength. For an ideal capacitor, leakage resistance would be infinite and ESR would be zero.

- **Breakdown strength:** Unlike resistors, capacitors do not have maximum power dissipation ratings. Instead, they have maximum voltage ratings. The **breakdown strength** of the dielectric will set an upper limit on how large of a voltage may be placed across a capacitor before it is damaged.

Breakdown strength is measured in volts per unit distance, thus, the closer the plates, the less voltage the capacitor can withstand. For example, halving the plate distance doubles the capacitance but also halves its voltage rating.

- **Capacitor Styles and Packaging:** Unlike resistors, whose physical size relates to their power rating and not their resistance value, the physical size of a capacitor is related to both its capacitance and its voltage rating

Modest surface mount capacitors can be quite small while the power supply filter capacitors commonly used in consumer electronics devices such as an audio amplifier can be considerably larger than a D cell battery



For large capacitors, the capacitance value and voltage rating are usually printed directly on the case. Some capacitors use “MFD” which stands for “microfarads”. While a capacitor color code exists, rather like the resistor color code, it has generally fallen out of favor. For smaller capacitors a numeric code is used that echoes the color code. Typically it consists of a three digit number such as “152”.

The first two digits are the precision portion and the third digit is the power of ten multiplier. The result is in picofarads. Thus, 152 is 1500 pf.



Figure 8.8

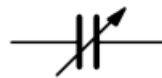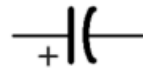Capacitor schematic symbols (top-bottom): non-polarized, polarized, variable.



- Capacitor Data Sheet:

Metallized Polypropylene Film Capacitor

Series : **ECWH(A)**

Non-inductive construction using metallized polypropylene film with flame retardant epoxy resin coating



Features

- Small size
- Excellent electrical characteristics
- Low loss
- Low Hum Sound Noise
- Flame retardant epoxy resin coating
- RoHS directive compliant

Recommended applications


- General resonance circuit

Specifications

Category temp. range (Including temperature-rise on unit surface)	- 40 °C to +105 °C	
Rated voltage	800 V.DC	1600 V.DC
Capacitance range	0.010 μ F to 0.047 μ F	0.0010 μ F to 0.047 μ F
Capacitance tolerance	± 3 % (H)	± 3 % (H), ± 5 % (J)
Dissipation factor ($\tan \delta$)	$\tan \delta \leq 0.1$ % (20 °C, 1 kHz)	
Withstand voltage	Between terminals : Rated volt. (V.DC) $\times$ 150 %, 60 s	
Insulation resistance (IR)	IR $\geq$ 30000 M Ω (20 °C, 500 V.DC, 60 s)	

* In case of applying voltage in alternating current (50 Hz or 60 Hz sine wave) to a capacitor with DC rated voltage, please refer to the page of "Permissible voltage (R.M.S) in alternating current corresponding to DC rated voltage".

Dimensions

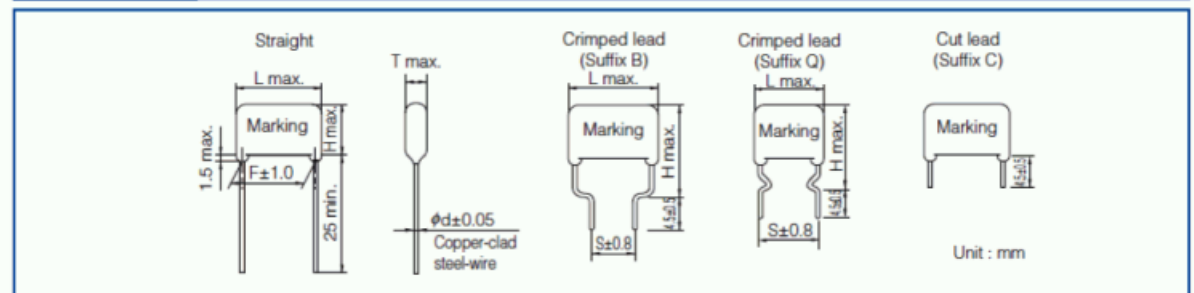

- **Capacitors in Series and in Parallel:** Multiple capacitors placed in series and/or parallel do not behave in the same manner as resistors. Placing capacitors in parallel increases overall plate area, and thus increases capacitance,

Therefore capacitors in parallel add in value, behaving like resistors in series. In contrast, when capacitors are placed in series, it is as if the plate distance has increased, thus decreasing capacitance. Therefore capacitors in series behave like resistors in parallel. Their value is found via the reciprocal of summed reciprocals or the product-sum rule.


If a circuit contains nothing but a voltage source in parallel with a group of capacitors, the voltage will be the same across all of the capacitors, just as it is in a resistive parallel circuit. If the circuit instead consists of multiple capacitors that are in series with a voltage source

the voltage will divide between them in inverse proportion. In other words, the larger the capacitance, the smaller its share of the applied voltage. The voltages can also be found by first determining the series equivalent capacitance. The total charge may then be determined using the applied voltage.

Finally, the individual voltages are computed from

$$V = \frac{Q}{C}.$$

Consider

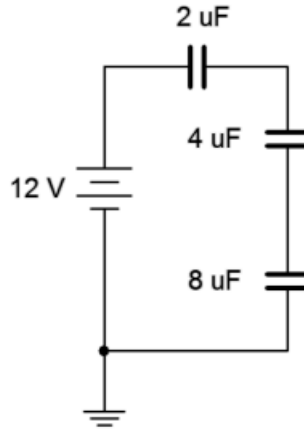

We have

$$C_{\text{total}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} = 1.143\mu F.$$

Hence,

$$Q = VC = 12V(1.143)\mu F = 13.71\mu C.$$

Charge is constant across all of the series capacitors, so

$$\begin{aligned} V_{2\mu F} &= \frac{13.71}{2} = 6.855V, \\ V_{4\mu F} &= \frac{13.71}{4} = 3.427V, \\ V_{8\mu F} &= \frac{13.71}{8} = 1.714V. \end{aligned}$$

The sum of the three voltages is 12 volts (within rounding error) and verifies KVL as expected.

- **Note:** While it may be tempting to try, do not attempt to verify the operation of Example 8.3 in the laboratory using a standard DMM. The reason is because the internal resistance of a typical digital voltmeter is many orders of magnitude lower than the leakage resistance of the capacitors. As a result, charge will be transferred to the meter, ruining the measurement. It would be akin to trying to measure the voltages across a string of resistors, each in excess of $100\text{ M}\Omega$, with a meter whose internal resistance is $1\text{ M}\Omega$. The meter's resistance dominates the parallel combination and causes excessive loading which ruins the measurement. A special sort of voltmeter, an electrostatic voltmeter or electrometer, is needed for these types of measurements. These are sometimes referred to as non-charge transfer meters.
- **Current-Voltage Relationship:** The fundamental current-voltage relationship of a capacitor is not the same as that of resistors. Capacitors do not so much resist current; it is more productive to think in terms of them reacting to it. The current through a capacitor is equal to the capacitance times the rate of change of the capacitor voltage with respect to time (i.e., its slope). That is, the value of the voltage is not important, but rather how quickly the voltage is changing. Given a fixed voltage, the capacitor current is zero and thus the capacitor behaves like an open. If the voltage is changing rapidly, the current will be high and the capacitor behaves more like a short. Expressed as a formula


$$i = C \frac{dv}{dt}.$$


Note that i is the current flowing through the capacitor. From this, we see

$$\frac{dv}{dt} = \frac{i}{C}.$$

If a capacitor is fed by a constant current source, the voltage will rise at a constant rate (dv/dt). It is continuously depositing charge on the plates of the capacitor at a rate of I , which is equivalent to Q/t . As long as the current is present, feeding the capacitor, the voltage across the capacitor will continue to rise. A good analogy is if we had a pipe pouring water into a tank, with the tank's level continuing to rise. This process of depositing charge on the plates is referred to as charging the capacitor.


Figure 8.15
Capacitor with current source.

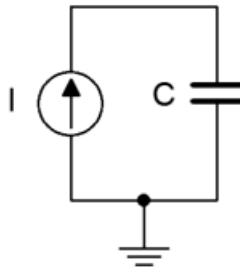

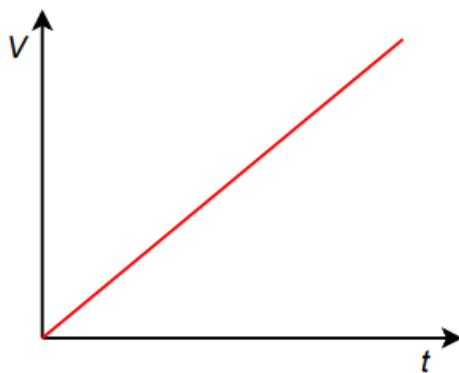

As time progresses, the voltage across the capacitor increases with a positive polarity from top to bottom. With a theoretically perfect capacitor and source, this would continue forever, or until the current source was turned off. In reality, this line would either begin to deflect horizontally as the source reached its limits, or the capacitor would fail once its breakdown voltage was reached. The slope of this line is dictated by the size of the current source and the capacitance

Consider

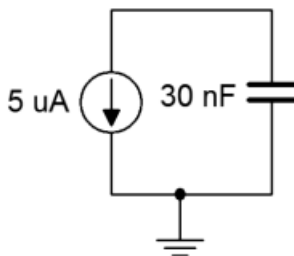

We wish to determine the rate of change of voltage across the capacitor, and determine the capacitors voltage 10 ms after power is switched on.

$$\frac{dv}{dt} = \frac{i}{C} = \frac{-5\mu A}{30nF} = -166.7 \frac{V}{s}.$$

So, after 10 ms, we see

$$-166.7(10) = -1.667V.$$

This is assuming it is completely uncharged when power is applied.

- **Limit:** If a capacitor is driven by a fixed current source, the voltage across it rises at the constant rate of i/C . There is a limit to how quickly the voltage across the capacitor can change. An instantaneous change means that dv/dt is infinite, and thus, the current driving the capacitor would also have to be infinite (an impossibility). This is not an issue with resistors, which obey Ohm's law, but it is a limitation of capacitors. Therefore we can state a particularly important characteristic of capacitors:

"The voltage across a capacitor cannot change instantaneously."

Note that instantaneous change means the voltage changes in zero time. Thus, the rate becomes infinitely large. This would force the current i to also be infinite.


This observation will be key to understanding the operation of capacitors in DC circuits.

- **Initial and Steady-State Analysis of RC Circuits:** When analyzing resistor-capacitor circuits, always remember that capacitor voltage cannot change instantaneously. If we assume that a capacitor in a circuit is not initially charged, then its voltage must be zero.


The instant the circuit is energized, the capacitor voltage must still be zero. If there is no voltage across the device, then it is behaving like a short circuit. We call this the initial state. Thus, we have our first rule regarding RC circuits:

"For DC analysis, initially capacitors appear as shorts"

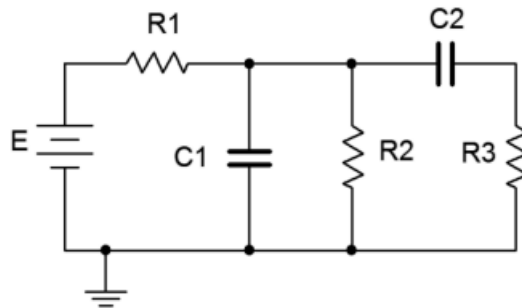Assume that C_1 and C_2 are initially uncharged and there is no voltage across them.



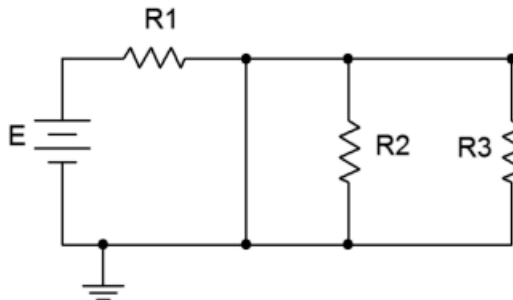The instant power is applied, the two capacitors appear as short circuits. If we redraw the circuit for this instant in time



Given this equivalent, we can see that shorting C_2 places R_2 and R_3 in parallel, however, they are both shorted out by C_1 . This leaves only R_1 left in the circuit along with the source, E . At this point, currents will begin to flow, and thus begin charging up the capacitors. As the capacitor voltages rise, the current will begin to decrease, and eventually the capacitors will stop charging. At that point no further current will be flowing, and thus the capacitor will behave like an open. We call this the **steady-state condition** and we can state our second rule:

"At steady-state, capacitors appear as opens."


Current decreases as a capacitor charges because the voltage building up across the capacitor's plates grows closer to the supply voltage, reducing the effective voltage difference that pushes electrons through the circuit

The current flowing into a capacitor is directly proportional to how fast its voltage changes over time ($i = C \frac{dv}{dt}$). As the capacitor approaches full charge, the voltage changes more slowly (

$$\frac{dv}{dt}$$

approaches zero), which forces the current down to zero.

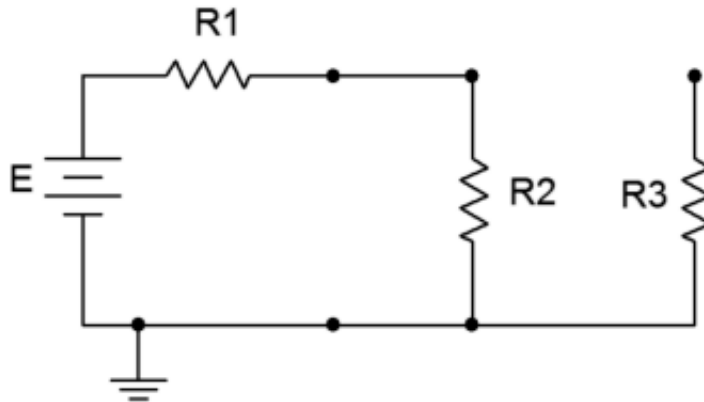
at steady-state both capacitors behave as opens



This leaves E to drop across R_1 and R_2 . This will create a simple voltage divider. The steady-state voltage across C_1 will equal that of R_2 . As C_2 is also open, the voltage across R_3 will be zero while the voltage across C_2 will be the same as that across R_2 .

In reality, practical capacitors can be thought of as an ideal capacitance in parallel with a very large (leakage) resistance, so there will be a limit to this performance.

Consider

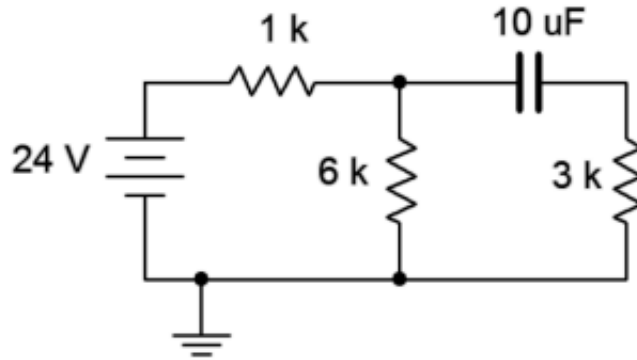

Initially, the capacitor is treated as a short. Thus,


$$V_{6k} = 24 - \frac{24}{6k || 3k + 1k}(1000) = 16V.$$

When the capacitor is fully charged, we treat it as an open. Thus,

$$V_{6k} = 24 - \frac{24}{1k + 6k}(1000) = 20.57V.$$

Remark: A capacitor acts like a short circuit only at the exact moment $t = 0$ when it is completely uncharged, and transitions gradually into an open circuit as the voltage across it builds up

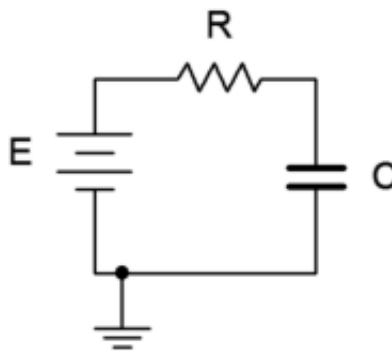- **Transient Response of RC Circuits:** The question remains, “What happens between the time the circuit is powered up and when it reaches steady-state?” This is known as the transient response



The key to the analysis is to remember that capacitor voltage cannot change instantaneously. Assuming the capacitor is uncharged, the instant power is applied, the capacitor voltage must be zero. Therefore all of the source voltage drops across the resistor. This creates the initial current, and this current starts to charge the capacitor


According to Kirchhoff's voltage law, as the capacitor voltage begins to increase, the resistor voltage must decrease because the sum of the two must equal the fixed source voltage. This means that the circulating current must also decrease

This, in turn, means that the rate of capacitor voltage increase begins to slow. As the capacitor voltage continues to increase, less voltage is available for the resistor, causing further reductions in current, and a further slowing of the rate of capacitor voltage change. Eventually, the capacitor voltage will be nearly equal to the source voltage.

This will result in a very small potential across the resistor and an equally small current, slowing subsequent capacitor voltage increases to a near standstill.

Theoretically, the capacitor voltage approaches the source voltage but never quite equals it.

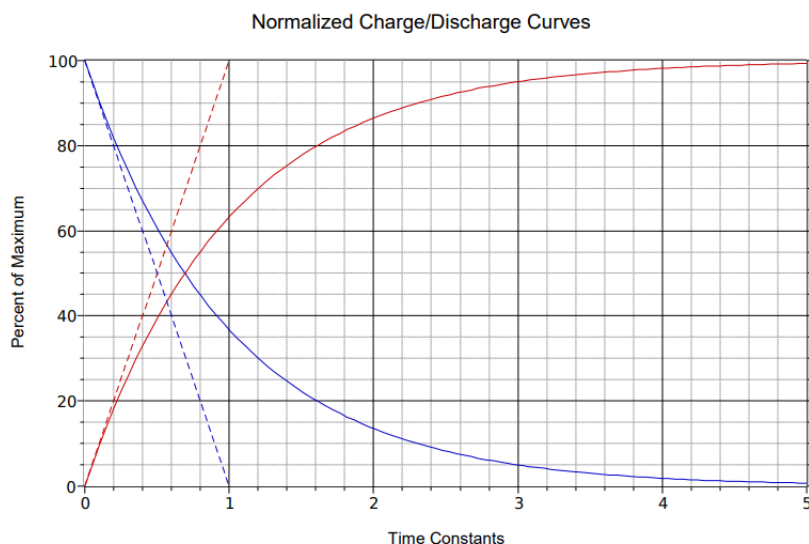Similarly, the current drops to near zero, but never completely turns off.



The dashed red line represents the initial rate of change of capacitor voltage. This trajectory is what would be expected if an ideal current source drove the capacitor. As noted previously, the rate of voltage change versus times is equal to i/C , and therefore in this case, $E/(RC)$. If the initial rate of change were to continue unabated, the source voltage, E , would be reached in RC seconds. Consequently, RC is referred to as the charge **time constant** and is denoted by τ . Thus

$$\tau = RC.$$

As noted, once the capacitor begins to charge, the current begins to decrease and the capacitor voltage curve begins to fall away from the initial trajectory. The solid red curve represents the capacitor voltage. Notice that after five time constants the capacitor is nearly fully charged and the circuit is considered to be in steady-state

"Steady-state is reached in approximately five time constants."

This sort of recursively dependent operation is characteristic of exponential functions. The equation for the capacitor's voltage charging curve is:

$$V_C(t) = E \left(1 - e^{-\frac{t}{\tau}} \right).$$

The dashed blue line shows the initial slope of current change. The solid blue curve shows the circulating current (and by extension of Ohm's law, the resistor voltage). The equation for this curve, which follows the general shape e^{-t} is


$$I(t) = \frac{E}{R} e^{-\frac{t}{\tau}},$$

$$V_R(t) = E e^{-\frac{t}{\tau}}.$$

Once power is removed or bypassed, the stored charge on the capacitor will dissipate through any associated resistor(s) creating a discharge current which will end with the capacitor voltage drained back to zero. During the discharge phase, both the capacitor's voltage and current will follow the solid blue curve

The discharge time constant may be different from the charge times constant, depending on the associated resistances.

Consider

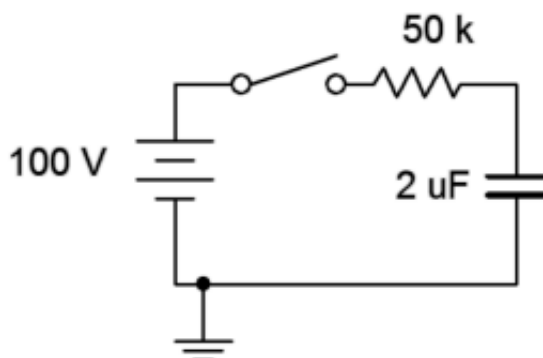

Assume the switch is closed at time $t = 0$. Determine the charging time constant, the amount of time after the switch is closed before the circuit reaches steady-state, and the capacitor voltage at $t = 0$, $t = 50$ milliseconds and $t = 1$ second. Assume the capacitor is initially uncharged.

The time constant is

$$\tau = RC = 50k\Omega \cdot 2\mu F = 100ms.$$

Steady-state will be reached in five time constants, or 500 milliseconds. So,

$$V_C(0) = 0V,$$

$$V_C(1) = 100V.$$

Also,

$$V_C(50) = 100V \left(1 - e^{-\frac{50}{100}} \right) \approx 39.35V.$$